

Electric Circuit 1  
Al-Anbar University



**LECTURE 02**  
**ENERGY AND POWER-OHMS**  
**LAW KIRCHOFFS CURRENT**  
**LAW**



## Topics

- ▶ Energy and power in electric circuits
- ▶ Ohm's Law
- ▶ Kirchhoff's Current Law



**After finishing this lecture, you should be able to:**

- ▶ Understand the relation between power and energy
- ▶ Understand the passive sign convention
- ▶ Use the passive sign convention in power calculation
- ▶ Determine if the power is actually absorbed or delivered
- ▶ Verify power conservation
- ▶ Use the passive sign convention in Ohm's Law
- ▶ Apply Kirchhoff's Current Law at a node
- ▶ Apply Kirchhoff's Current Law at a supernode



## Electric Energy and Power

The power  $p(t)$  *absorbed by* an electric element and the energy  $w(t)$  in the *same* element are related by

$$p(t) = \frac{dw(t)}{dt}$$

Unit of  $w$  is Joule (J)

Unit of  $p$  is Watt (W)

Unit of  $t$  is second (s)



## Direction of Power Flow

If the energy  $w(t)$  *increases* with time [  $w(t)$  has a +ve slope ], then

$\frac{dw(t)}{dt} > 0 \Rightarrow p(t) > 0 \Rightarrow$  power is being actually absorbed by the element

If the energy  $w(t)$  *decreases* with time [  $w(t)$  has a -ve slope ], then

$\frac{dw(t)}{dt} < 0 \Rightarrow p(t) < 0 \Rightarrow$  power is being actually delivered by the element

$w(t)$  increases  $\Leftrightarrow$  power being absorbed

$w(t)$  decreases  $\Leftrightarrow$  power being delivered




## Relation with v-i

The power  $p(t)$  can be expressed in terms of  $v(t)$  and  $i(t)$

$$p(t) = \frac{dv}{dq} \frac{dq}{dt} = v(t)i(t)$$

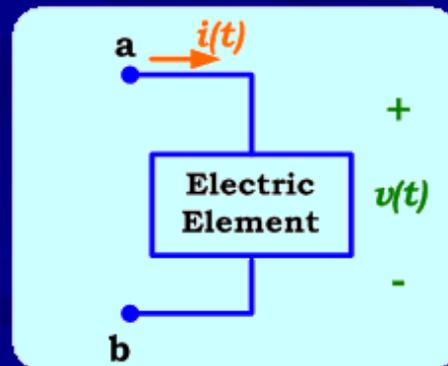The above relation applies *only* when the current enters the element from the (+) terminal and leaves the (-) terminal, as shown below






## Relation with v-i

If the current enters the element from the ( - ) terminal and leaves the ( + ) terminal, as shown below, then we have

$$p(t) = -v(t)i(t)$$

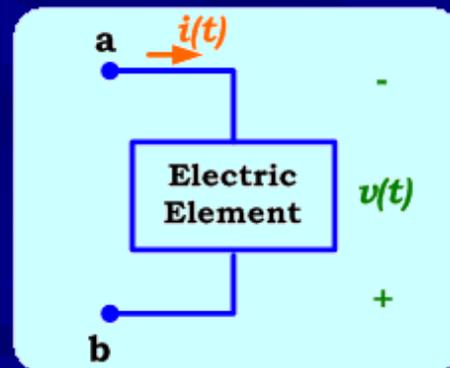
In this case it is *necessary* to insert a minus sign in the power expression, in order to have consistent results.






## Relation with v-i

### Summary

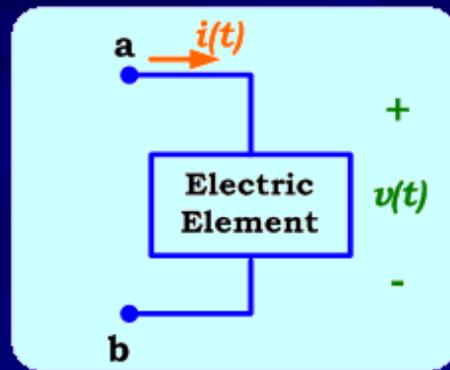


$$p = +v i$$

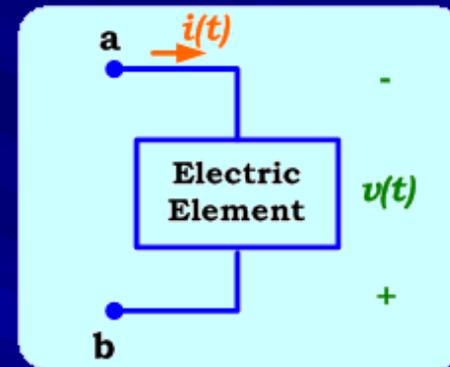


$$p = -v i$$
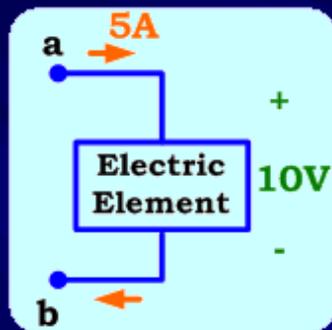
## Example 1


Calculate the power absorbed by each element in the given circuits. State whether the power is *actually absorbed* or *delivered* by the element.




(a)

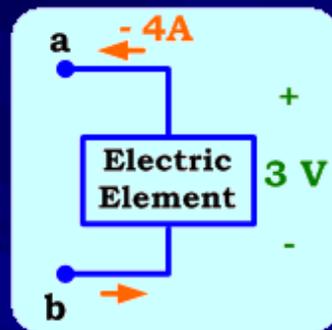

(b)

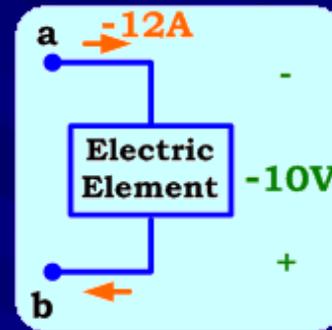

(c)

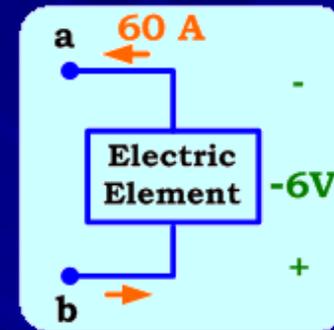

(d)

Solution:

$$(a) \quad p = +i v = +(5)(10) = +50 \text{ W} \quad \Rightarrow p > 0 \quad \Rightarrow \text{power actually absorbed}$$

$$(b) \quad p = -i v = -(-4)(3) = +12 \text{ W} \quad \Rightarrow p > 0 \quad \Rightarrow \text{power actually absorbed}$$

$$(c) \quad p = -i v = -(-12)(-10) = -120 \text{ W} \quad \Rightarrow p < 0 \quad \Rightarrow \text{power actually delivered}$$

$$(d) \quad p = +i v = +(60)(-6) = -360 \text{ W} \quad \Rightarrow p < 0 \quad \Rightarrow \text{power actually delivered}$$



## Equivalent Statements

The following statements are equivalent

Power *absorbed by* the element

Power *delivered to* the element

Power *dissipated by* the element

Power *consumed by* the element

The following statements are also equivalent


Power *delivered by* the element

Power *generated by* the element

The symbol  $p$  will be reserved for the power absorbed by the element
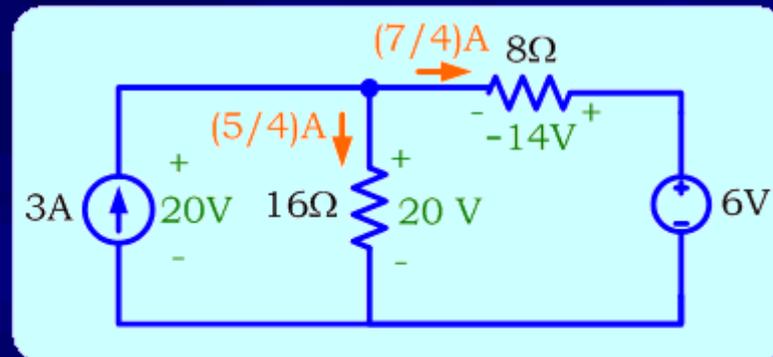
## Example 2

- Calculate the power absorbed by each element in the given circuit.
- Show that the total power dissipated is equal to the total power generated



Solution:

$$(i) P_{6V} = +iv = +(7/4)(6) = 10.5W \Rightarrow \text{dissipated}$$

$$P_{3A} = -iv = -(3)(20) = -60W \Rightarrow \text{generated}$$

$$P_{16\Omega} = +iv = +(5/4)(20) = 25W \Rightarrow \text{dissipated}$$

$$P_{8\Omega} = -iv = -(7/4)(-14) = 24.5W \Rightarrow \text{dissipated}$$

$$(ii) \sum P_{dis} = 10.5 + 25 + 24.5 = 60W$$

$$\sum P_{gen} = 60W$$

$$\sum P_{dis} = \sum P_{gen}$$




## Ohm's Law

The voltage  $v(t)$  and current  $i(t)$  in a resistor  $R$  are related by

$$v = iR$$

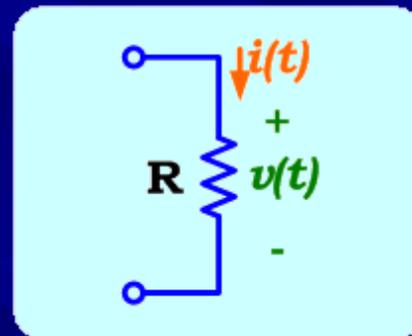The above relation is valid *only if* current  $i(t)$  enters the resistor from the ( + ) terminal and leaves the ( - ) terminal, as shown below






## Ohm's Law

If the current  $i(t)$  enters the resistor from the (-) terminal and leaves the (+) terminal, as shown below, then Ohm's law *must be* change to

$$v = -iR$$

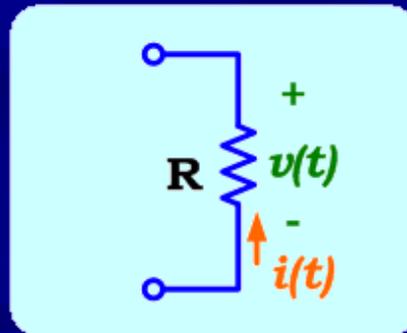
In this case it is necessary to insert a minus sign in the expression, in order to have consistent results.






## Ohm's Law

### Summary

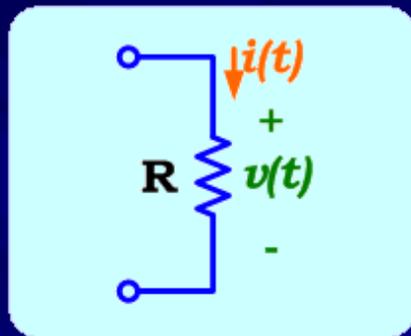

$$v = iR$$

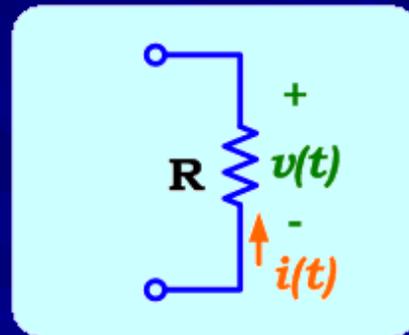

$$v = -iR$$



## The Passive Sign Convention


The use of the  $\pm$  signs in the Ohm's law and the power expression is known as the *passive sign convention*

$$i(t) \text{ enters the } (+) \text{ terminal} \Rightarrow p = +vi \quad \text{and} \quad v = +iR$$

$$i(t) \text{ enters the } (-) \text{ terminal} \Rightarrow p = -vi \quad \text{and} \quad v = -iR$$
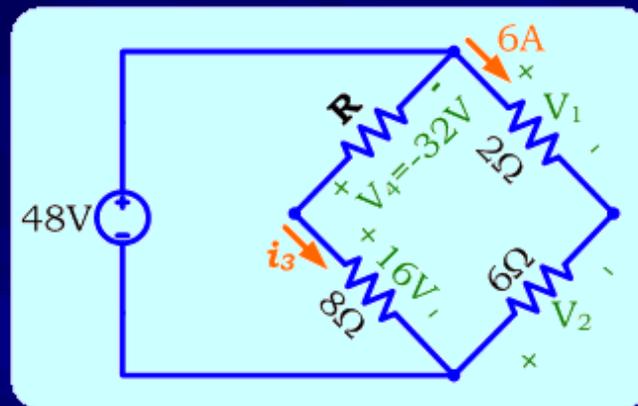
## Example

Calculate the unknown quantities in the following circuit



Solution:

$$v_1 = +(6)(2) = 12\text{V}$$

$$i_3 = + \frac{16}{8} = 2\text{A}$$


$$v_2 = -(6)(6) = -36\text{V}$$

$$R = - \frac{v_4}{i_3} = - \frac{(-32)}{2} = 16\Omega$$


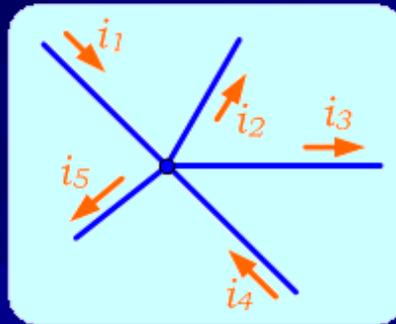
## Kirchhoff's Current Law (KCL)

The sum of currents *entering* a node (interconnection of two or more branches) is equal to the sum of currents *leaving* that node



$$i_1 + i_4 = i_2 + i_3 + i_5$$


Equivalent Statement of KCL:

The algebraic sum of currents entering a node (currents entering the node is taken as positive) is equal to zero

$$i_1 - i_2 - i_3 + i_4 - i_5 = 0$$
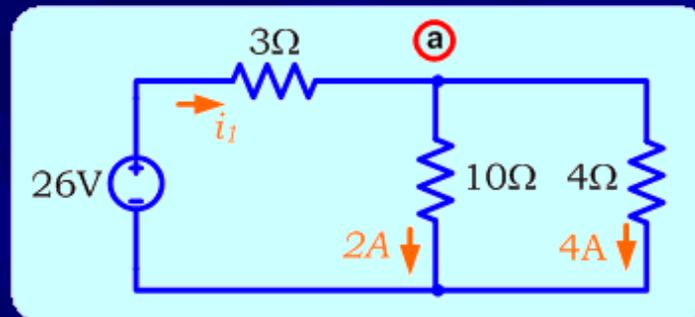
## Example 1

Calculate the unknown current in the following circuit




Solution:

$$\text{KCL at node a} \Rightarrow i_1 = 2 + 4 = 6 \text{ A}$$
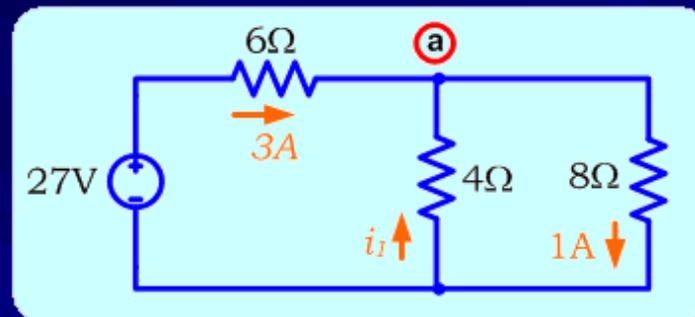
## Example 2

Calculate the unknown current in the following circuit



Solution:

$$\text{KCL at node a} \Rightarrow 3 + i_1 = 1 \Rightarrow i_1 = -2A$$


Alternatively,

$$\text{KCL at node a} \Rightarrow 3 + i_1 - 1 = 0 \Rightarrow i_1 = -2A$$


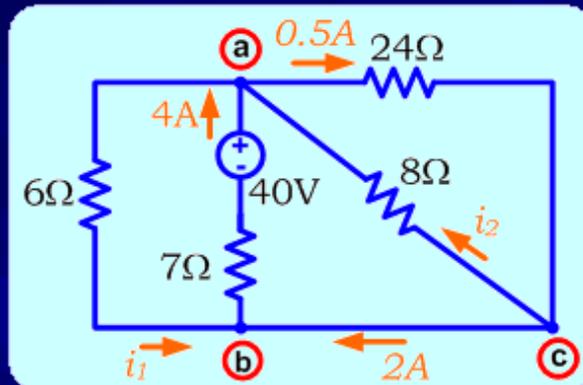
### Example 3

Calculate the unknown currents in the following circuit



Solution:

$$\text{KCL at node b} \quad \Rightarrow \quad i_1 - 4 + 2 = 0 \quad \Rightarrow \quad i_1 = 2A$$


$$\text{KCL at node c} \quad \Rightarrow \quad 0.5 - i_2 - 2 = 0 \quad \Rightarrow \quad i_2 = -1.5A$$

$$\text{Check KCL at node a} \quad \Rightarrow \quad -i_1 + 4 + i_2 - 0.5 = -(2) + 4 + (-1.5) - 0.5 = -4 + 4 = 0$$


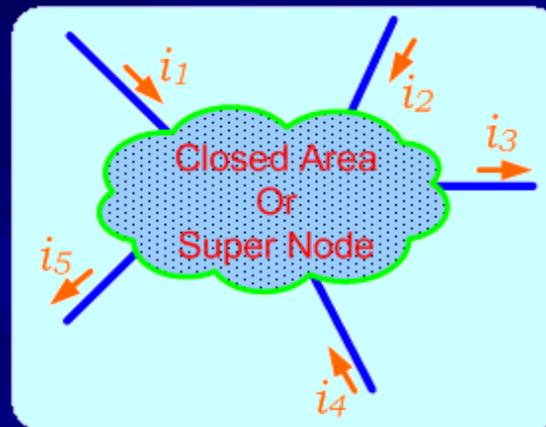
## Supernode

KCL is also applicable to a *closed area* (super node)




The algebraic sum of currents entering a super node is equal to zero

$$i_1 + i_2 - i_3 + i_4 - i_5 = 0$$
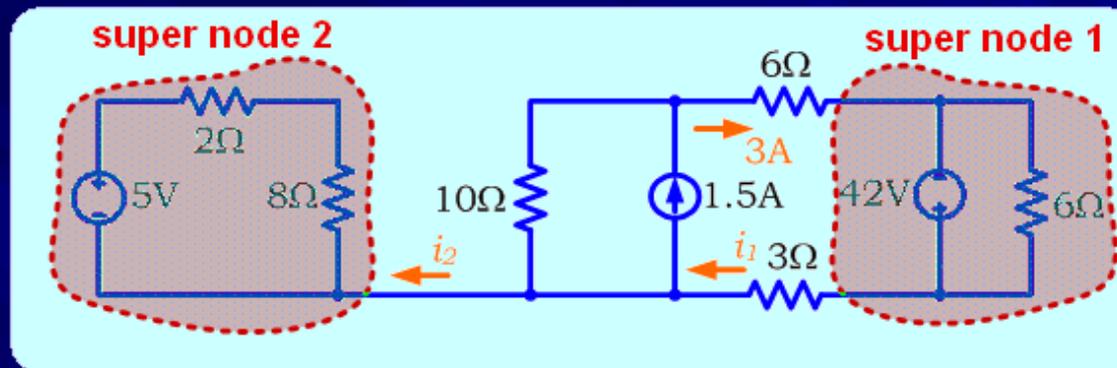
## Example 4

Calculate the unknown currents in the circuit shown below




Solution:

$$\text{KCL at super node 1} \Rightarrow 3 - i_1 = 0 \Rightarrow i_1 = 3A$$

$$\text{KCL at super node 2} \Rightarrow i_2 = 0 \Rightarrow i_2 = 0A$$

## Self Test

In the circuit shown below, calculate:

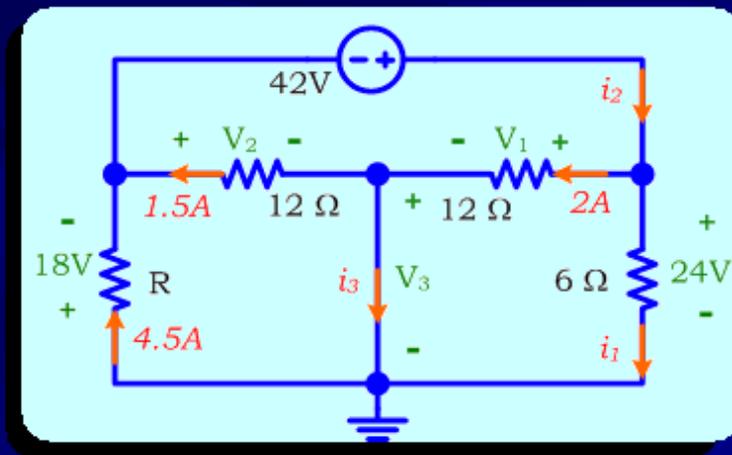

(a)  $i_1$

- A  $i_1 = 144A$
- B  $i_1 = -4A$
- C  $i_1 = 4A$
- D  $i_1 = 1/4 A$
- E  $i_1 = -1/4 A$

