

0.1 Star Delta Transformation

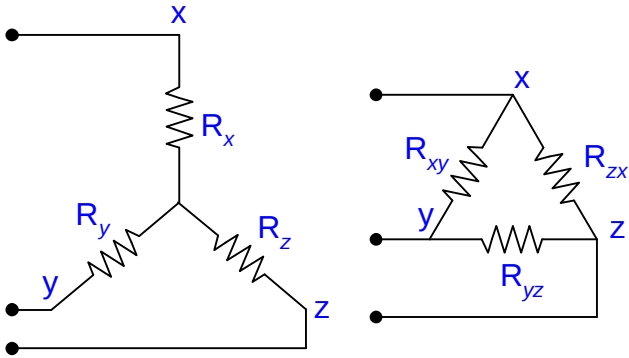


Figure 1

$$R_x + R_y = \frac{R_{xy}(R_{yz} + R_{zx})}{R_{xy} + R_{yz} + R_{zx}} \quad (1)$$

$$R_y + R_z = \frac{R_{yz}(R_{zx} + R_{xy})}{R_{xy} + R_{yz} + R_{zx}} \quad (2)$$

$$R_z + R_x = \frac{R_{zx}(R_{xy} + R_{yz})}{R_{xy} + R_{yz} + R_{zx}} \quad (3)$$

Equation (1)-(2)

$$R_x - R_z = \frac{R_{xy}R_{zx} - R_{yz}R_{zx}}{R_{xy} + R_{yz} + R_{zx}} \quad (4)$$

Equation (3)+(4)

$$2R_x = \frac{2R_{xy}R_{zx}}{R_{xy} + R_{yz} + R_{zx}}$$

$$R_x = \frac{R_{xy}R_{zx}}{R_{xy} + R_{yz} + R_{zx}} \quad (5)$$

Similarly

$$R_y = \frac{R_{yz}R_{yx}}{R_{xy} + R_{yz} + R_{zx}} \quad (6)$$

$$R_z = \frac{R_{zy}R_{zx}}{R_{xy} + R_{yz} + R_{zx}} \quad (7)$$

Star to Delta Transformation

$$R_x R_y = \frac{R_{xy}^2 R_{zx} R_{yz}}{(\sum R_{xy})^2}$$

$$R_y R_z = \frac{R_{yz}^2 R_{yx} R_{zx}}{(\sum R_{xy})^2}$$

$$R_z R_x = \frac{R_{zx}^2 R_{yx} R_{yz}}{(\sum R_{xy})^2}$$

$$R_x R_y + R_y R_z + R_z R_x = \frac{R_{xy} R_{yz} R_{zx} (R_{xy} + R_{yz} + R_{zx})}{(\sum R_{xy})^2}$$

$$R_x R_y + R_y R_z + R_z R_x = \frac{R_{xy} R_{yz} R_{zx} (R_{xy} + R_{yz} + R_{zx})}{(\sum R_{xy})^2}$$

$$R_x R_y + R_y R_z + R_z R_x = \frac{R_{xy} R_{yz}}{\sum R_{yz}} R_{zx} = R_x R_{yz}$$

$$R_{yz} = \frac{R_x R_y + R_y R_z + R_z R_x}{R_x}$$

$$R_{yz} = R_y + R_z + \frac{R_y R_z}{R_x} \quad (8)$$

$$R_{xy} = R_x + R_y + \frac{R_x R_y}{R_z} \quad (9)$$

$$R_{zx} = R_z + R_x + \frac{R_z R_x}{R_y} \quad (10)$$

Q 1) 2020-Aug (2018 scheme ECE) 2020-Aug (2018 scheme EE) 2017-June **Determine the Input resistance between PQ using star-delta transformation**

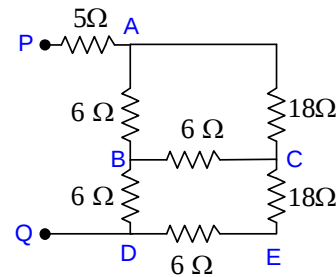


Figure 2

Solution:

In the given circuit 6 Ω, 6 Ω and 18 connected between A,B and C are in delta connection, convert this into star network. The details are as shown in Figure 3

$$R_A = \frac{R_{AB} \times R_{AC}}{\sum R_{AB}}$$

$$R_A = \frac{6 \times 18}{30} = 3.6\Omega$$

$$R_B = \frac{6 \times 6}{30} = 1.2\Omega$$

$$R_C = \frac{6 \times 18}{30} = 3.6\Omega$$

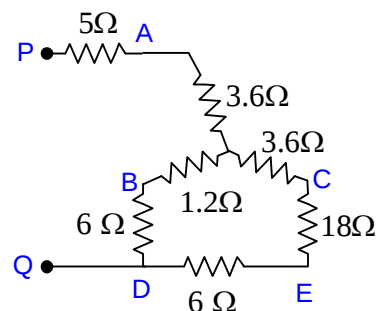


Figure 3

In the circuit $5\ \Omega$ and $3.6\ \Omega$ are in series, $6\ \Omega$ and $1.2\ \Omega$ are in series and $3.6\ \Omega$, $18\ \Omega$ and $6\ \Omega$ are in series.

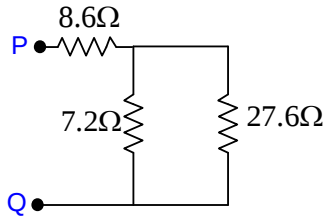


Figure 4

$7.2\ \Omega$, $27.6\ \Omega$ are in parallel, which is in series with $8.6\ \Omega$. The net resistance is.

$$\begin{aligned} R_{PQ} &= 8.6 + \frac{7.2 \times 27.6}{7.2 + 27.6} \\ &= 8.6 + 5.71 \\ &= 14.31\ \Omega \end{aligned}$$

Q 2) For the circuit shown in Figure shown in Figure 5 determine the equivalent resistance between any two terminals.

Solution:

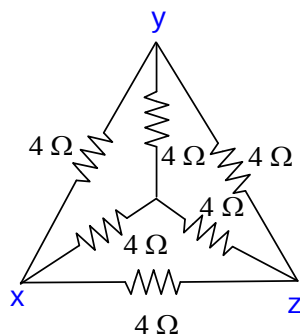


Figure 5

Solution:

In the given $4, 4, 4,$ and Ω are in star network, convert this star network to delta network

$$\begin{aligned} R_{xy} &= R_x + R_y + \frac{R_x \times R_y}{R_z} = 8 + 4 = 12\ \Omega \\ R_{xy} &= 4 + 4 + \frac{4 \times 4}{4} = 8 + 4 = 12\ \Omega \\ R_{yz} &= 4 + 4 + \frac{4 \times 4}{4} = 8 + 4 = 12\ \Omega \\ R_{zx} &= 4 + 4 + \frac{4 \times 4}{4} = 8 + 4 = 12\ \Omega \end{aligned}$$

As shown in the Figure 6, by looking by any two terminals $12\ \Omega$ is parallel with $4\ \Omega$

$$= \frac{12 \times 4}{12 + 4} = 3\ \Omega$$

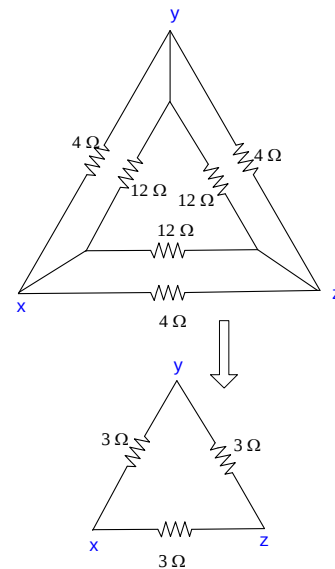


Figure 6

By looking from XZ terminal the $3\ \Omega$ resistance is in parallel with series connection of $3\ \Omega$ and $3\ \Omega$ resistance.

$$R_{XZ} = \frac{3 \times 6}{3 + 6} = 2\ \Omega$$

Q 3) For the circuit shown in Figure shown in Figure 7 determine the equivalent resistance between (1) A and B and (2) A and N.

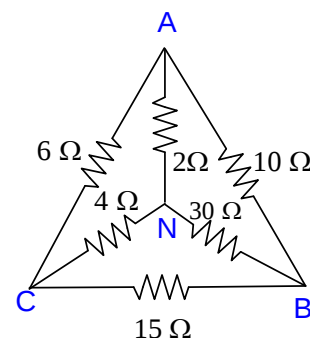


Figure 7

Solution:

Convert the internal star network to delta

network

$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{AB} = 2 + 30 + \frac{2 \times 30}{4} = 32 + 15 = 47 \Omega$$

$$R_{BC} = 4 + 30 + \frac{4 \times 30}{2} = 34 + 60 = 94 \Omega$$

$$R_{CA} = 4 + 2 + \frac{4 \times 2}{30} = 6 + 0.266 = 6.266 \Omega$$

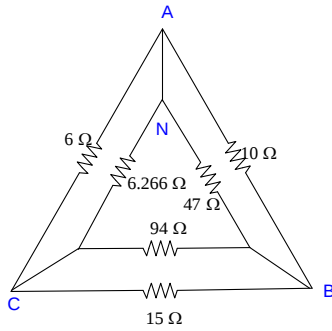


Figure 8

In the circuit 10 Ω is parallel with 47 Ω

$$= \frac{10 \times 47}{10 + 47} = 8.245 \Omega$$

Similarly 94 Ω is parallel with 15 Ω

$$= \frac{94 \times 15}{94 + 15} = 12.93 \Omega$$

Similarly 6 Ω is parallel with 6.266 Ω

$$= \frac{6 \times 6.266}{6 + 6.266} = 3.06 \Omega$$

The details are as shown in Figure ??

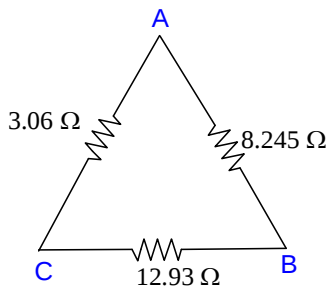


Figure 9

While looking from terminal AB the resistances 12.93 Ω and 3.06 Ω are in series and this resistance is parallel with 8.245 Ω

$$= 12.93 + 3.06 = 16 \Omega$$

$$R_{AB} = \frac{8.245 \times 16}{8.245 + 16} = 5.44 \Omega$$

(ii) The resistance between A and N is

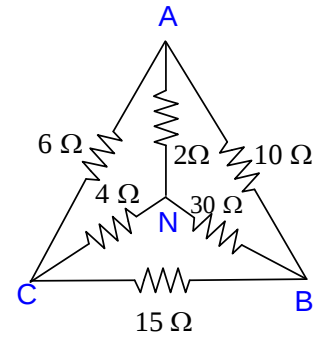


Figure 10

From the Figure 10 by looking from the terminal resistance between A and N, there is a delta network between NCB which is replaced by star network.

$$R_x = \frac{R_{xy} R_{xz}}{R_{xy} + R_{yz} + R_{zx}}$$

$$R_B = \frac{30 \times 15}{30 + 15 + 4} = 9.18$$

$$R_C = \frac{4 \times 15}{30 + 15 + 4} = 1.225$$

$$R_N = \frac{30 \times 4}{30 + 15 + 4} = 2.5$$

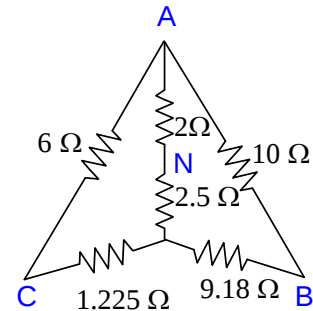


Figure 11

In the network of 6 Ω and 1.225 Ω are in series, 10 Ω and 9.18 Ω are in series. The details are as shown in Figure 12

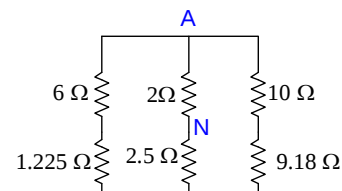


Figure 12

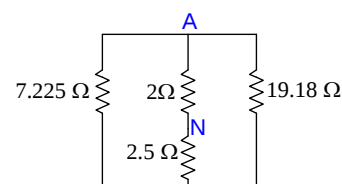


Figure 13

The resistances 7.225 Ω and 19.18 Ω are in

parallel

$$= \frac{7.225 \times 19.18}{7.225 + 19.18} = 5.25\Omega$$

The details are as shown in Figure 14

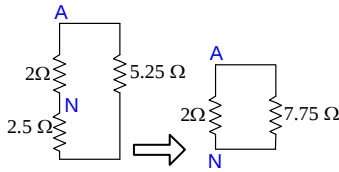


Figure 14

The resistances 2.5Ω and 5.25Ω are in series. The resistances 2Ω and 7.75Ω are in parallel and the net resistance between A and N is

$$= \frac{2 \times 7.75}{2 + 7.75} = 1.59\Omega$$

Q 4) Determine the equivalent resistance between terminals A and B

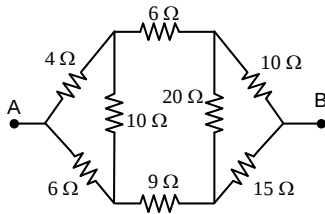


Figure 15

Solution:

$$R_A = \frac{4 \times 6}{4 + 6} = 1.2\Omega$$

$$R_B = \frac{4 \times 10}{4 + 10} = 2\Omega$$

$$R_C = \frac{6 \times 10}{6 + 10} = 3\Omega$$

$$R_A = \frac{10 \times 15}{10 + 15} = 3.33\Omega$$

$$R_B = \frac{10 \times 20}{10 + 20} = 4.44\Omega$$

$$R_C = \frac{20 \times 15}{20 + 15} = 6.667\Omega$$

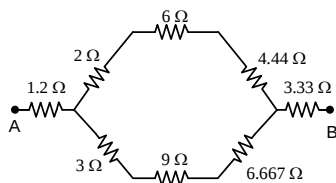


Figure 16

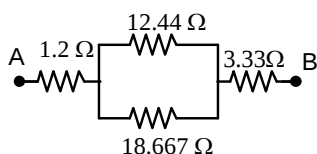


Figure 17

$$\begin{aligned} R_{AB} &= 1.2 + \frac{12.44 \times 18.667}{12.44 + 18.667} + 3.3\Omega \\ &= 1.2 + \frac{232.217}{31.107} + 3.3\Omega \\ &= 1.2 + 7.446 + 3.3 = 11.94\Omega \end{aligned}$$

Q 5) 2018-Dec (2010 scheme) Find the resistance of the circuit shown in Figure shown in Figure 5 between A and B

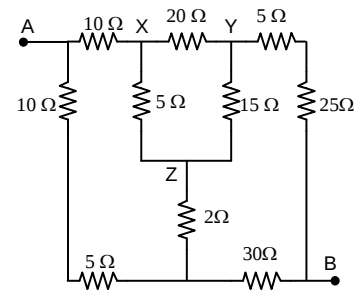


Figure 18

Solution:

In the given network 18 there is delta network between xyz and it is replaced by star network.

$$R_X = \frac{20 \times 5}{20 + 5} = 2.5\Omega$$

$$R_Y = \frac{20 \times 15}{20 + 15} = 7.5\Omega$$

$$R_Z = \frac{15 \times 5}{15 + 5} = 1.875\Omega$$

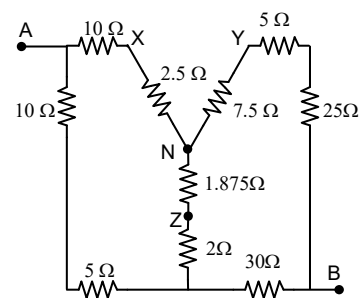


Figure 19

In the circuit 19, 10Ω and 2.5Ω are in series, similarly 5Ω and 7.5Ω are in series. The details are as shown in Figure 20

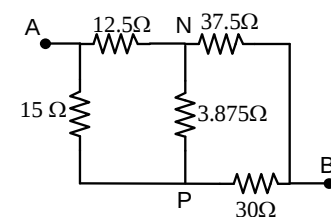


Figure 20

In the circuit 20 at NPB 37.5Ω 3.875Ω and 30 are in delta connection, convert into star network. The details are as shown in Figure 21

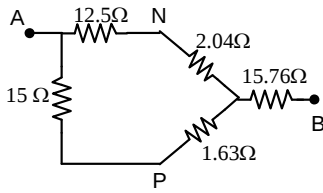


Figure 21

In the circuit 21, 12.5Ω , 2.045Ω are in series, similarly 1.635Ω 15Ω are in series. The details are as shown in Figure 22

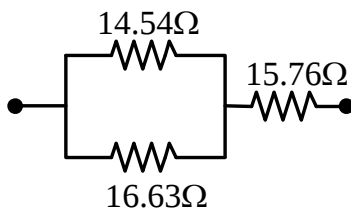


Figure 22

In the circuit 22 14.54Ω , 16.63Ω are in parallel, which is in series with similarly 15.76Ω . The net resistance between AB is.

$$\begin{aligned} R_{AB} &= 15.76 + \frac{14.54 \times 16.63}{14.54 + 16.63} \\ &= 15.76 + 7.76 \\ &= 23.52 \Omega \end{aligned}$$

Q 6) For the circuit shown in Figure shown in Figure 5 determine the current i using star delta transformation.

Solution:

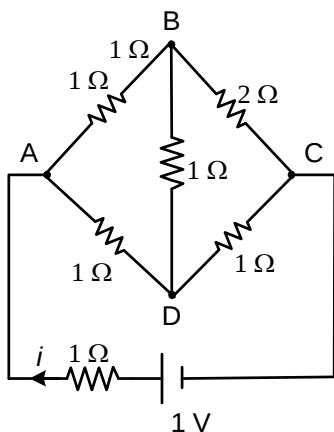


Figure 23

As shown in Figure 23 there is delta network between ABC, convert this to star network

$$R_A = \frac{1 \times 1}{1 + 1 + 1} = 0.333 \Omega$$

$$R_B = \frac{1 \times 1}{1 + 1 + 1} = 0.333 \Omega$$

$$R_C = \frac{1 \times 1}{1 + 1 + 1} = 0.333 \Omega$$

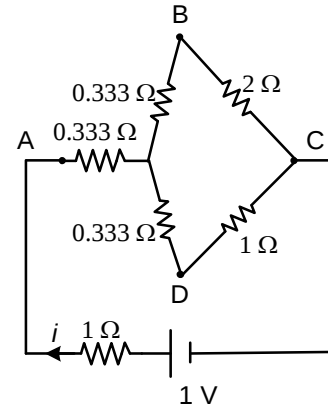


Figure 24

The resistances 0.333Ω and 2Ω are in series and 0.333Ω and 1Ω are in series.

The resistances 2.333Ω and 1.333Ω are in parallel its equivalent resistance is

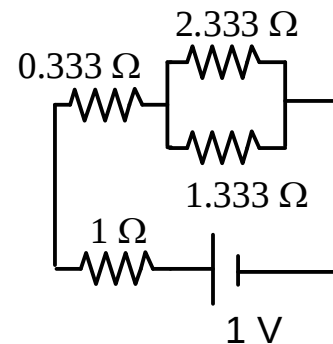


Figure 25

$$= \frac{2.333 \times 1.333}{2.333 + 1.333} = \frac{3.109}{3.666} = 0.848 \Omega$$

Total network resistance is $1 + 0.333 + 0.848 = 2.181 \Omega$

$$I = \frac{1}{2.181} = 0.458 A$$

Q 7) Calculate the current in the 40Ω resistance of the circuit shown in Figure shown in Figure 5 using star delta transformation.

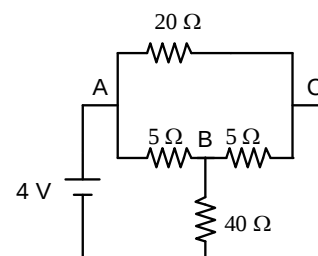


Figure 26

Solution:

As shown in Figure 23 there is delta network between ABC, convert this to star network

$$R_A = \frac{20 \times 5}{30} = 3.333\Omega$$

$$R_B = \frac{5 \times 5}{30} = 0.833\Omega$$

$$R_C = \frac{20 \times 5}{30} = 3.333\Omega$$

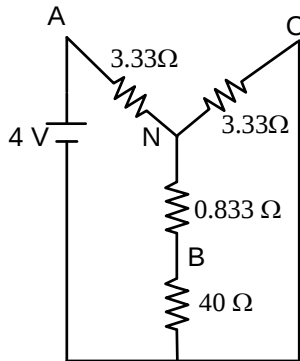


Figure 27

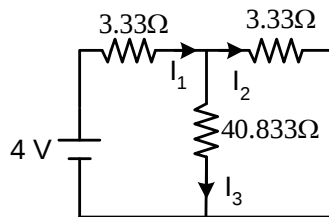


Figure 28

The total resistance of the network is

$$= 3.333 + \frac{40.833 \times 3.333}{40.833 + 3.333} = 3.333\Omega$$

$$= 3.333 + \frac{136}{44.163} = 3.333 + 3.08 + \Omega$$

$$= 6.41\Omega$$

The total current flowing in the network is

$$I_1 = \frac{4}{6.41} = 0.624A$$

Using branch current division method the current in 40 Ω is

$$I_3 = 0.624A \frac{3.333}{44.163} = 0.047A$$

Q 8) Determine the currents supplied by the each battery using star-delta transformation

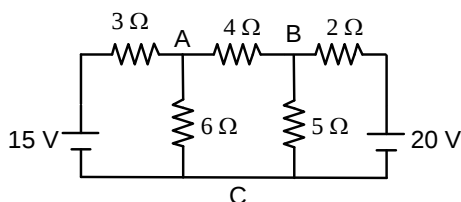


Figure 29

Solution:

As shown in Figure 29 there is delta network between ABC, convert this to star network

$$R_A = \frac{4 \times 6}{15} = 1.6\Omega$$

$$R_B = \frac{4 \times 5}{15} = 1.3\Omega$$

$$R_C = \frac{6 \times 5}{15} = 2\Omega$$

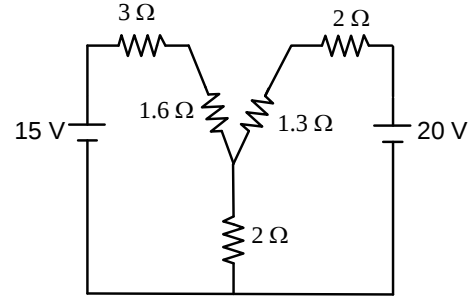


Figure 30

In the circuit 30, 3 Ω and 1.6 Ω are in series and also 2 Ω and 1.3 Ω are in series. The details are as shown in Figure 31

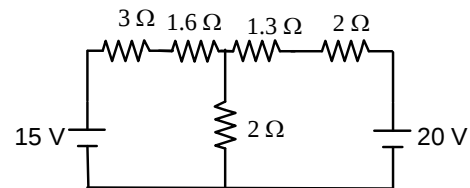


Figure 31

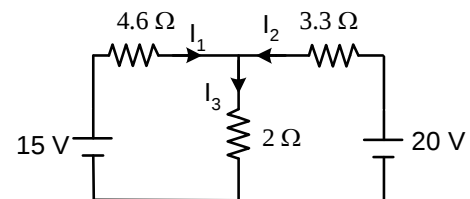


Figure 32

$$I_3 = I_1 + I_2$$

KVL for loop 1

$$15 - 4.6I_1 - 2I_3 = 0$$

$$15 - 4.6I_1 - 2I_1 - 2I_2 = 0$$

$$15 - 6.6I_1 - 2I_2 = 0$$

$$6.6I_1 + 2I_2 = 15$$

KVL for loop 2

$$20 - 3.3I_2 - 2I_3 = 0$$

$$20 - 3.3I_2 - 2I_1 - 2I_2 = 0$$

$$20 - 5.3I_2 - 2I_1 = 0$$

$$2I_1 + 5.3I_2 = 20$$

Simultaneous equations are

$$6.6I_1 + 2I_2 = 15 \quad (11)$$

$$2I_1 + 5.3I_2 = 20 \quad (12)$$

$$\Delta = \begin{vmatrix} 6.6 & 2 \\ 2 & 5.3 \end{vmatrix} = 6.6 \times 5.3 - (2 \times 2) = 34.98 - 4 = 30.98$$

$$i_1 = \frac{\begin{vmatrix} 15 & 2 \\ 20 & 5.3 \end{vmatrix}}{\Delta} = \frac{79.5 - 40}{32.96} = \frac{39.5}{30.98} = 1.275A$$

$$i_2 = \frac{\begin{vmatrix} 6.6 & 15 \\ 2 & 20 \end{vmatrix}}{\Delta} = \frac{132 - 30}{30.98} = \frac{102}{30.98} = 3.292A$$

The current supplied by each battery are 1.275A and 3.292A respectively

9). Find the equivalent resistance between A and B as shown in Figure 33

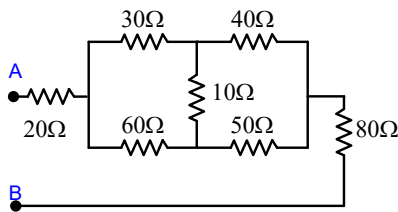


Figure 33

Solution:

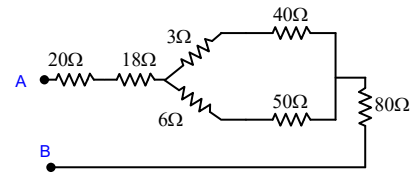


Figure 34

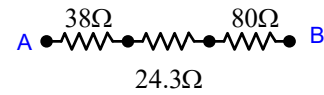
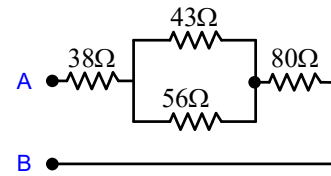


Figure 35

$$\begin{aligned} R_{AB} &= 1.87 + \frac{6.94 \times 3.55}{6.94 \times 3.55} \\ &= 38 + 24.3 + 80 = 142.3\Omega \end{aligned}$$

0.2 Question Papers

network

Question Papers

2019-Jan (2017 scheme ECE) Find the equivalent resistance between a and b as shown in Figure 36 using star delta transformation

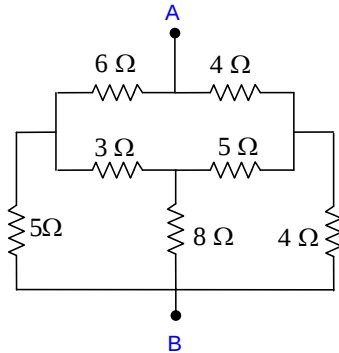


Figure 36: JAN-2019-Question Paper

Solution:

As shown in Figure 36 there is delta network between 8Ω 5Ω and 4Ω, convert this to star network

$$R_A = \frac{8 \times 5}{8 + 4 + 5} = 2.35\Omega$$

$$R_B = \frac{5 \times 4}{17} = 1.17\Omega$$

$$R_C = \frac{8 \times 4}{17} = 1.88\Omega$$

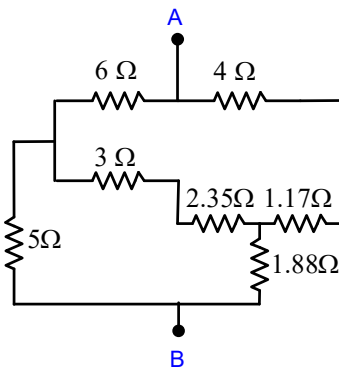


Figure 37

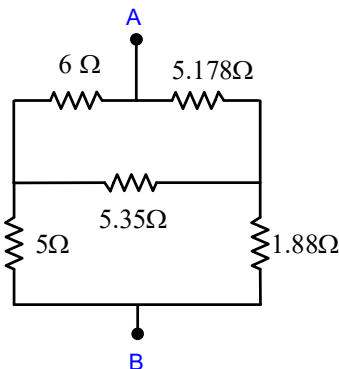


Figure 38

As shown in Figure 38 there is delta network between 6Ω 5.17Ω and 5.35 Ω, convert this to star

$$R_A = \frac{6 \times 5.17}{6 + 5.17 + 5.35} = 1.87\Omega$$

$$R_B = \frac{5.17 \times 5.35}{16.52} = 1.67\Omega$$

$$R_C = \frac{6 \times 5.35}{16.52} = 1.94\Omega$$

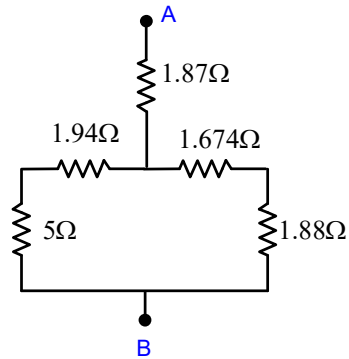


Figure 39

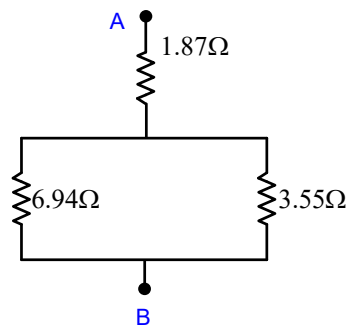


Figure 40

$$R_{AB} = 1.87 + \frac{6.94 \times 3.55}{6.94 + 3.55}$$

$$= 1.87 + 2.34 = 4.21\Omega$$

2019-DEC Determine the resistance between A and B of the network shown in Figure 41.

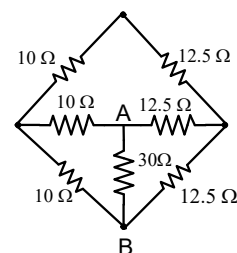


Figure 41: 2019-DEC

Solution:

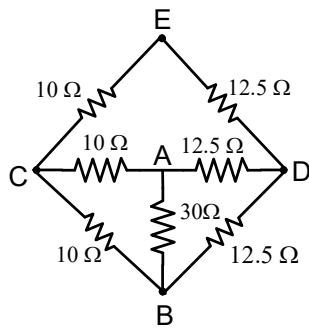


Figure 42

As shown in Figure 42 there is delta network between 2Ω 3Ω and 6Ω , convert this to star network

$$R_A = \frac{10 \times 30}{10 + 10 + 30} = 6\Omega$$

$$R_B = \frac{10 \times 30}{50} = 6\Omega$$

$$R_C = \frac{10 \times 10}{50} = 2\Omega$$

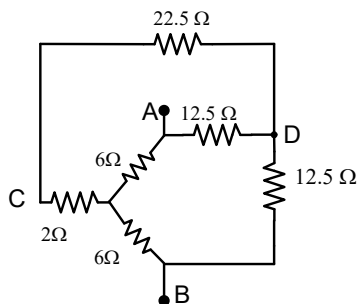


Figure 43

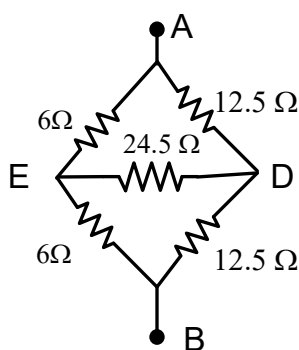


Figure 44

As shown in Figure 44 there is delta network between 6Ω 12.5Ω and 24.5Ω , convert this to star network

$$R_A = \frac{6 \times 12.5}{6 + 12.5 + 24.5} = 1.74\Omega$$

$$R_B = \frac{6 \times 24.5}{43} = 3.41\Omega$$

$$R_C = \frac{12.5 \times 24.5}{43} = 7.12\Omega$$

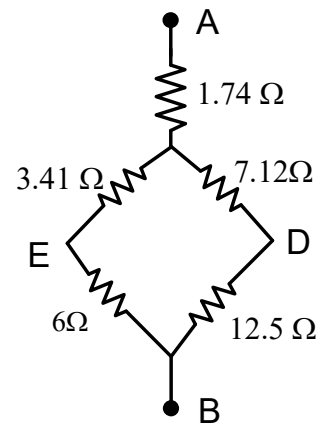


Figure 45

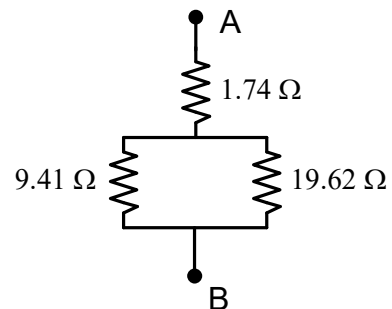


Figure 46

$$R_{AB} = 1.74 + \frac{9.41 \times 19.62}{9.41 + 19.62} = 1.74 + 6.36$$

$$= 8.1\Omega$$

Also by observation its a wheatstone bridge because the ratio is

$$\frac{12.5}{12.5} = \frac{6}{6} = 1$$

Hence no current flows between E D

$$R_{AB} = \frac{25 \times 12}{25 + 12} = 8.1\Omega$$

2019-DEC Determine the resistance between A and B of the network shown in Figure 41.

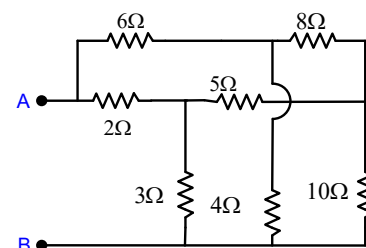


Figure 47: 2019-June-(2015-scheme-ECE)1

Solution:

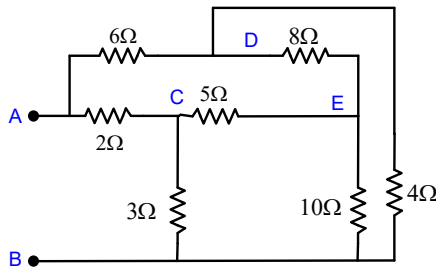


Figure 48

As shown in Figure 48 there is star network between 2Ω 3Ω and 5Ω , convert this to star network

$$R_{AB} = 2 + 3 + \frac{2 \times 3}{5} = 5 + 1.2 = 6.2\Omega$$

$$R_{AE} = 2 + 5 + \frac{2 \times 5}{3} = 7 + 3.3 = 10.3\Omega$$

$$R_{BE} = 5 + 3 + \frac{5 \times 3}{2} = 8 + 7.5 = 15.5\Omega$$

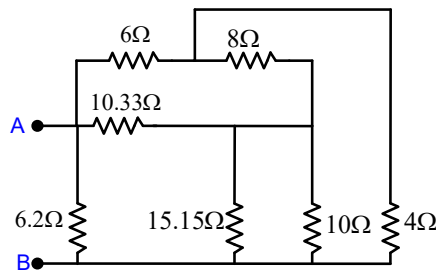


Figure 49

$$= \frac{10 \times 15.5}{10 + 15.5} = 6.07\Omega$$

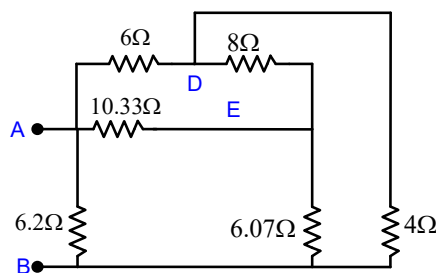


Figure 50

As shown in Figure 50 there is a delta network between 6.2Ω 10.33Ω and 6.07Ω , convert this to star network

$$R_A = \frac{6.2 \times 10.33}{6.2 + 10.33 + 6.07} = 2.83\Omega$$

$$R_B = \frac{6.2 \times 6.07}{22.6} = 1.67\Omega$$

$$R_E = \frac{6.07 \times 10.33}{22.6} = 2.77\Omega$$

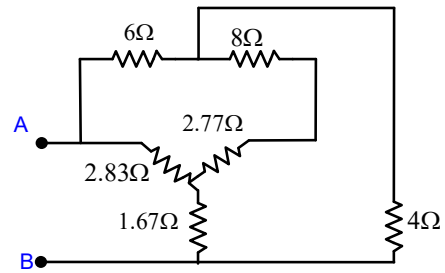


Figure 51

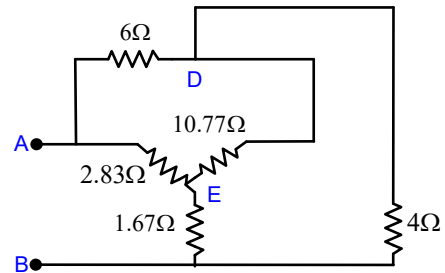


Figure 52

As shown in Figure 52 there is a delta network between 2.83Ω 6Ω and 10.77Ω , convert this to star network

$$R_A = \frac{2.83 \times 6}{19.6} = 0.87\Omega$$

$$R_E = \frac{2.83 \times 10.77}{19.6} = 1.55\Omega$$

$$R_D = \frac{10.77 \times 6}{19.6} = 3.3\Omega$$

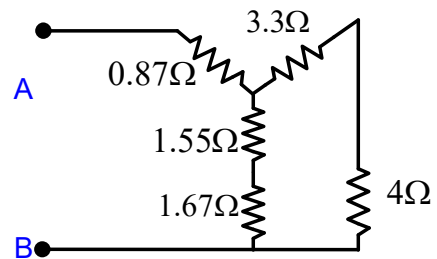


Figure 53

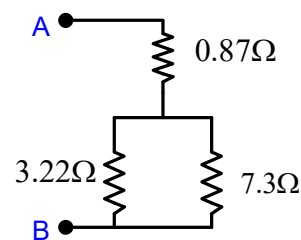


Figure 54

$$= 0.87 + \frac{3.22 \times 7.3}{3.22 + 7.3} = 0.87 + 2.23$$

$$= 3.1\Omega$$

2018-Dec, 2014-Dec Using star/delta transformation network determine the resistance between M and N of the network shown in Figure 55.

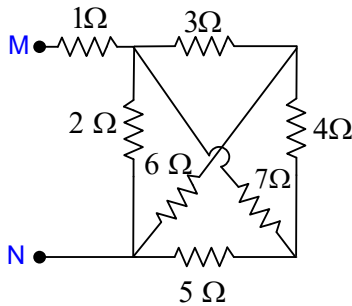


Figure 55: 2018-DEC-(2015-scheme-ECE)1

Solution:

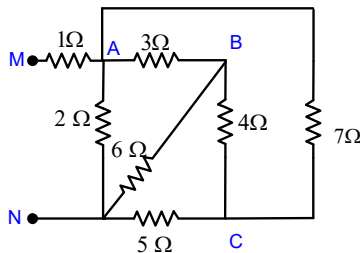


Figure 56

As shown in Figure 56 there is delta network between 2Ω , 3Ω and 6Ω , convert this to star network

$$R_A = \frac{2 \times 3}{2 + 3 + 6} = 0.545\Omega$$

$$R_B = \frac{3 \times 6}{11} = 1.636\Omega$$

$$R_C = \frac{6 \times 2}{11} = 1.1\Omega$$

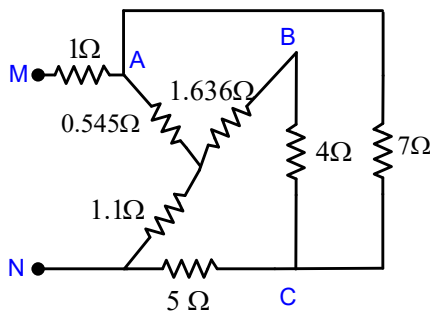


Figure 57

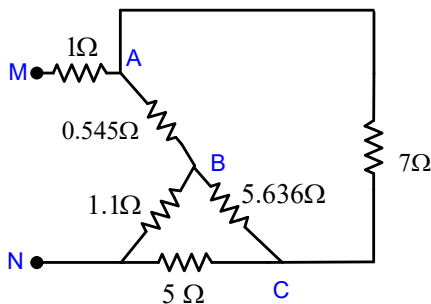


Figure 58

As shown in Figure 59 there is delta network between 1.1Ω , 5.636Ω and 5Ω , convert this to star

$$R_B = \frac{1.1 \times 5.636}{11.736} = 0.528\Omega$$

$$R_N = \frac{1.1 \times 5}{11.736} = 0.468\Omega$$

$$R_C = \frac{5.636 \times 5}{11.736} = 2.4\Omega$$

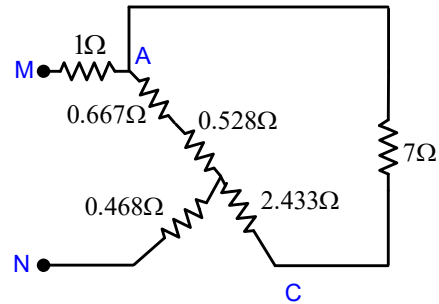


Figure 59

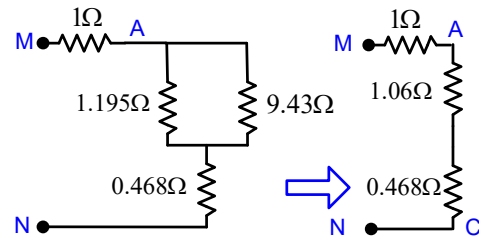


Figure 60

$$R_B = \frac{1.195 \times 9.43}{1.195 + 9.43} = 1.06\Omega$$

$$R_{MN} = 1 + 1.06 + 0.468 = 2.528\Omega$$

2015-Dec Find the equivalent resistance between A and B of the network shown in Figure 61 using Star-Delta transformation.

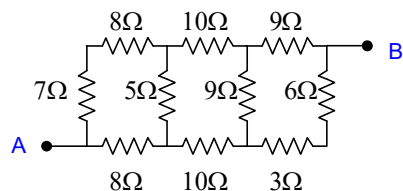


Figure 61: 2015-DEC

Solution:

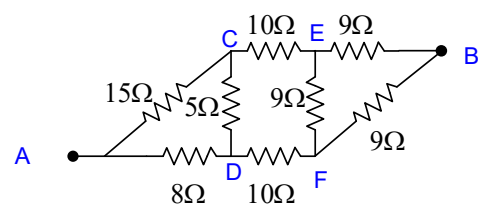


Figure 62

As shown in Figure 62 there is delta network between 15Ω , 8Ω and 5Ω , and there is delta network

between 9Ω 9Ω and 9Ω , convert this to star network

$$R_A = \frac{15 \times 8}{28} = 4.28\Omega$$

$$R_D = \frac{5 \times 8}{28} = 1.42\Omega$$

$$R_C = \frac{15 \times 5}{28} = 2.67\Omega$$

$$R_B = \frac{9 \times 9}{27} = 3\Omega$$

$$R_E = \frac{9 \times 9}{27} = 3\Omega$$

$$R_F = \frac{9 \times 9}{27} = 3\Omega$$

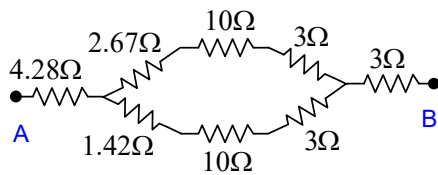


Figure 63

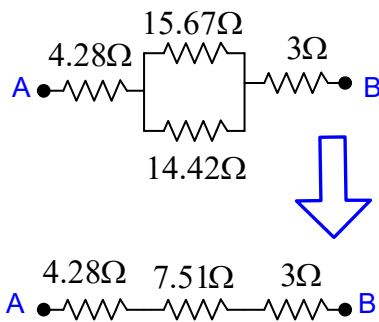


Figure 64

15.67 and 14.42 Ω are in parallel

$$= \frac{15.67 \times 14.42}{15.67 + 14.42} = 7.51\Omega$$

$$R_{AB} = 4.28 + 7.51 + 3 = 14.79\Omega$$

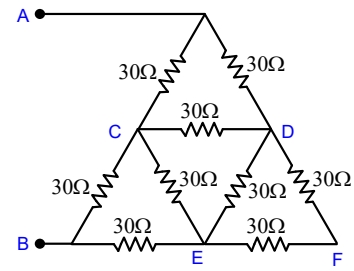


Figure 66: 2013-DEC1

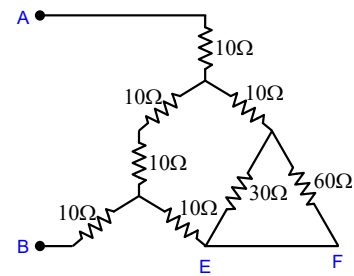


Figure 67: 2013-DEC1

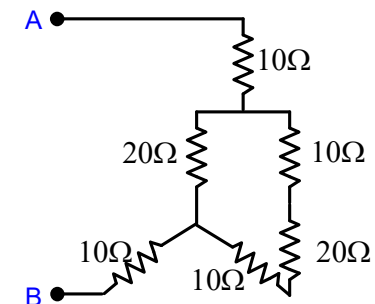


Figure 68: 2013-DEC1

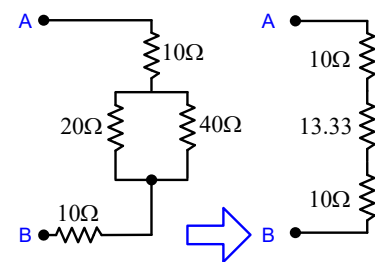


Figure 69: 2013-DEC1

2013-DEC1 Using star/delta transformation determine the resistance between M and N of the network shown in Figure 65.

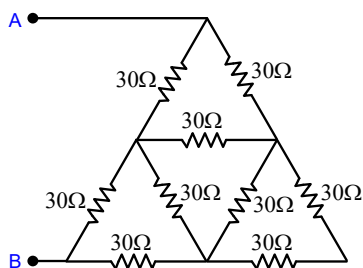


Figure 65: 2013-DEC1

Solution:

2008-June Using star/delta transformation determine the resistance between M and N of the network shown in Figure 70.

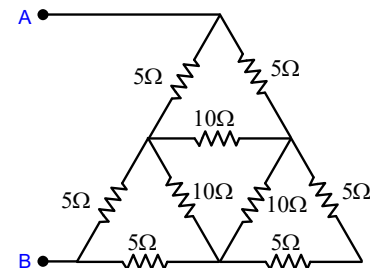


Figure 70: 2008-June

Solution:

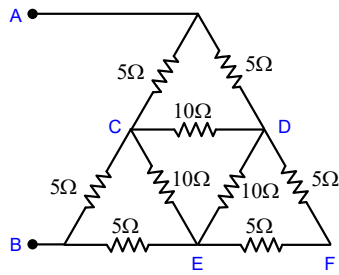


Figure 71: 2008-June

As shown in Figure 71 there is delta network between A C D 5Ω 5Ω and 10Ω , and there is delta network between B C E 5Ω 5Ω and 10Ω , convert this to star network

$$R_A = \frac{5 \times 5}{20} = 1.25\Omega$$

$$R_C = \frac{5 \times 10}{20} = 2.5\Omega$$

$$R_D = \frac{5 \times 10}{20} = 2.5\Omega$$

$$R_B = \frac{5 \times 5}{20} = 1.25\Omega$$

$$R_E = \frac{5 \times 10}{20} = 2.5\Omega$$

$$R_F = \frac{5 \times 10}{20} = 2.5\Omega$$

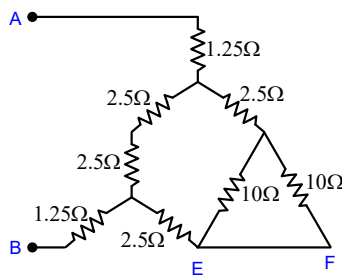


Figure 72: 2008-June22

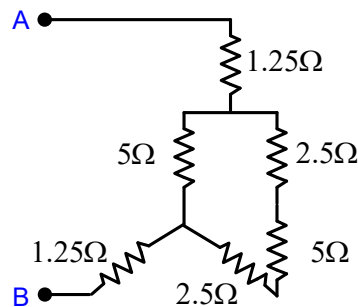


Figure 73: 2008-June23

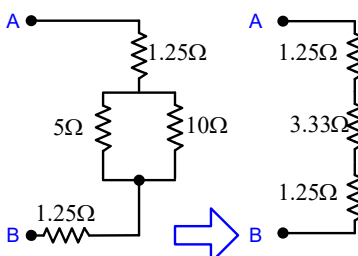


Figure 74: 2008-June24

$$\begin{aligned} R_{AB} &= 1.25 + 3.33 + 1.25 \\ &= 5.83\Omega \end{aligned}$$

2007-July Using star/delta transformation determine the resistance between A and B of the network shown in Figure 75.

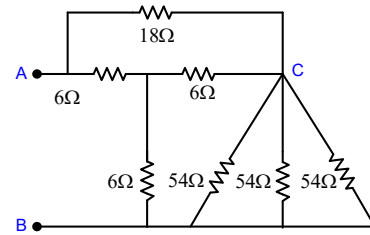


Figure 75: 2007-July

Solution:

As shown in Figure 75 there is star network between 6Ω 6Ω and 6Ω , convert this to star to delta network

$$R_{AB} = 6 + 6 + \frac{6 \times 6}{6} = 12 + 6 = 18\Omega$$

$$R_{AC} = 6 + 6 + \frac{6 \times 6}{6} = 12 + 6 = 18\Omega$$

$$R_{BC} = 6 + 6 + \frac{6 \times 6}{6} = 12 + 6 = 18\Omega$$

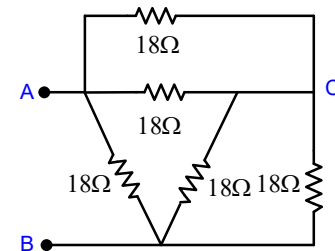


Figure 76: 2007-July

18Ω between AC and AB are in parallel

$$= \frac{18 \times 18}{36} = 9\Omega$$

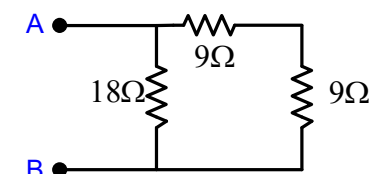


Figure 77: 2007-July

9Ω and 9Ω are in series which is in parallel with 18Ω

$$AB = 18 + \frac{9 \times 9}{18} = 18 + 4.5 = 22.5\Omega$$

Using star/delta transformation determine the resistance between A and B of the network shown in Figure 78.

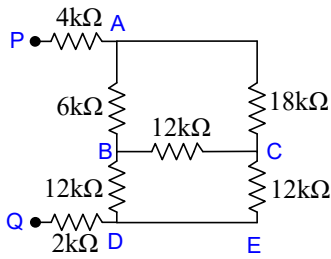


Figure 78

Solution:

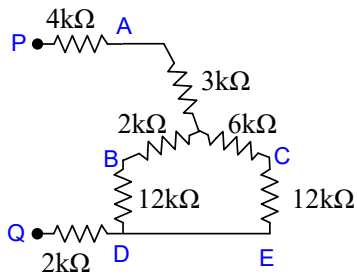


Figure 79

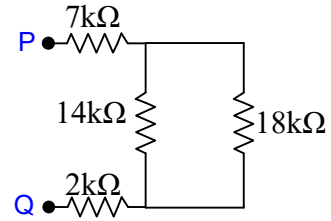


Figure 80

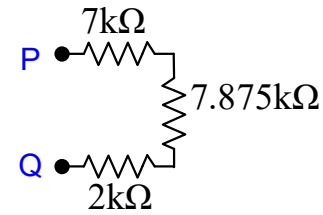


Figure 81

$$R_{PQ} = 7 + 7.785 + 2 = 16.785k\Omega$$