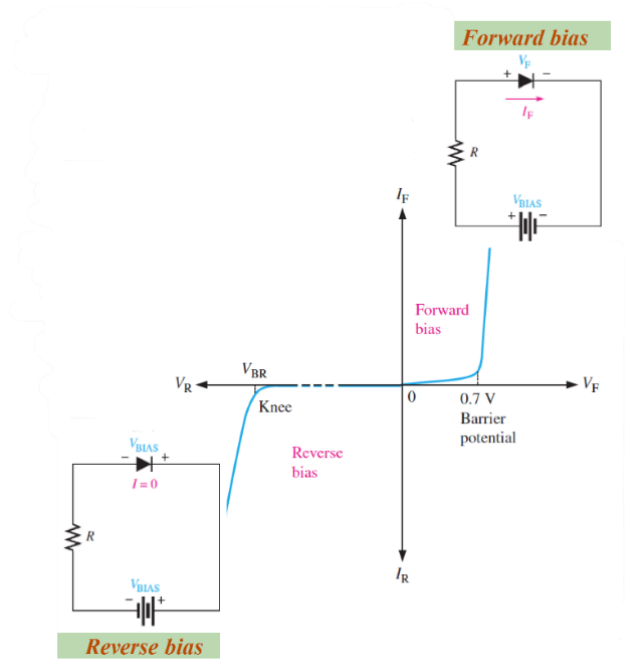


كلية الهندسة	الكلية
قسم الهندسة الكهربائية	القسم
Fundamentals of Electronics I	المادة باللغة الانجليزية
أسس الإلكترونيك ١	المادة باللغة العربية
الثانية	المرحلة الدراسية
حامد ردام حسين	اسم التدريسي
SEMICONDUCTOR DIODES	عنوان المحاضرة باللغة الانجليزية
ثنائيات أشباه الموصلات	عنوان المحاضرة باللغة العربية
6	رقم المحاضرة
Electronic Devices and Circuit Theory 11 th Edition by Robert L. Boylestad, Louis Nashelsky	المصادر والمراجع
Electronic Devices 9th Edition by Thomas L. Floyd	

Lecture 5: Diode Equivalent Circuits (Diode Models)

1. Diode Modelling

- In electronics, **diode modelling** refers to the mathematical models used to approximate the actual behavior of **real diodes** to enable calculations and circuit analysis.
- A diode's I-V curve is **nonlinear** (it is well described by the Shockley diode law).
- This nonlinearity complicates calculations in circuits involving diodes so simpler models are often required.



2. Shockley diode model

The Shockley diode equation relates the diode current (I_D) of an p-n junction diode to the diode voltage (V_D). This relationship is the diode *I-V characteristic*:

$$I_D = I_s(e^{kV_D/T_K} - 1)$$


I_s = reverse saturation current

$$k = 11,600/\eta$$


$\eta = 1$ for Ge and $\eta = 2$ for Si for below the knee of the curve,

$\eta = 1$ for both Ge and Si above the knee.

$$T_k = T_c + 273^0$$

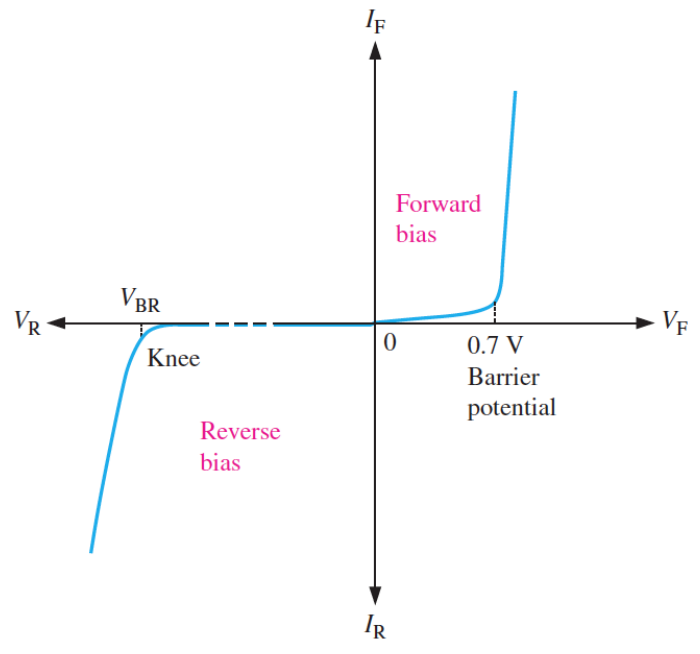


3. Diode Models

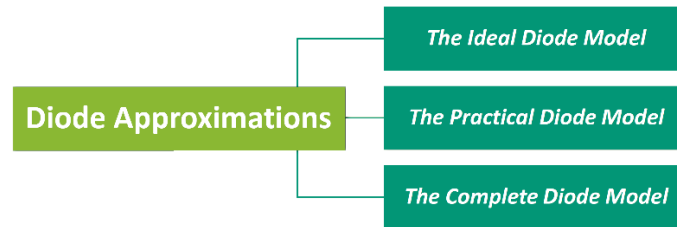

- Barrier potential
- Reverse current
- Dynamic resistance

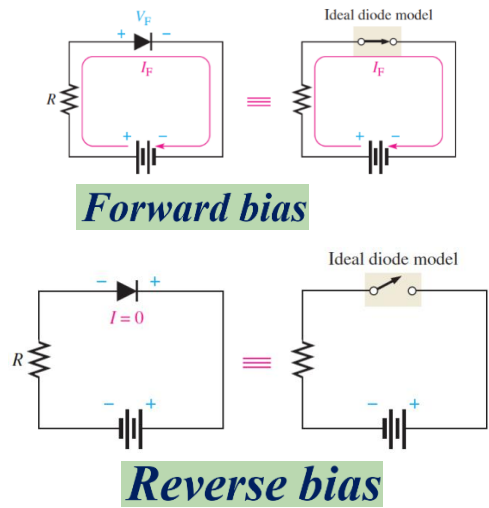4. The Ideal Diode Model

- The ideal model of a diode is the least accurate approximation and can be represented by a **simple switch**.
- When the diode is forward-biased, it ideally acts like a closed (on) switch
- When the diode is reverse-biased, it ideally acts like an open (off) switch.



- The diode is assumed to have a **zero voltage** across it when **forward-biased**, as indicated by the portion of the curve on the positive vertical axis.

$$V_F = 0 V$$

- The **forward current** is determined by the bias voltage and the limiting resistor using Ohm's law.


$$I_F = \frac{V_{BIAS}}{R_{LIMIT}}$$

- The **reverse current** is neglected

$$I_R = 0 A$$

- The **reverse voltage** equals the bias voltage.

$$V_R = V_{BIAS}$$

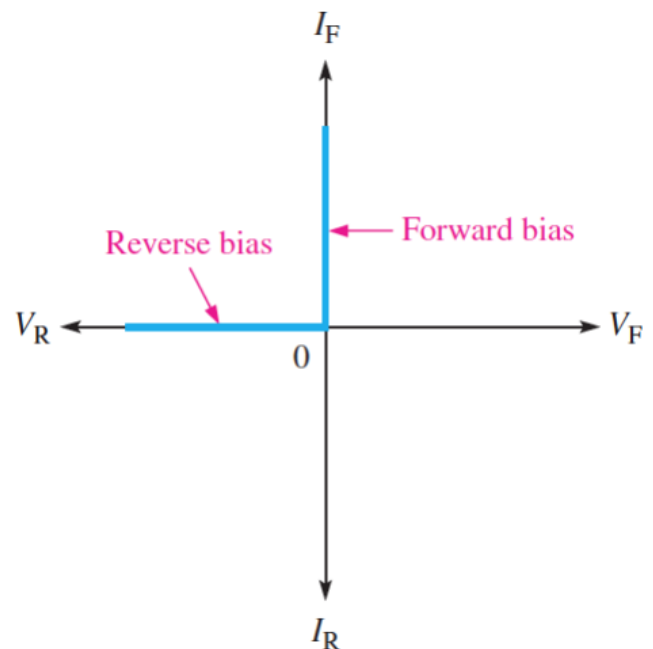

Ideal V-I characteristic curve

5. The Practical Diode Model

- The practical model includes the **barrier potential**.
- When the diode is **forward-biased**, it is equivalent to a closed switch in series with a small equivalent voltage source (V_F) equal to the barrier potential (0.7V) with the positive side toward the anode.

Note: This equivalent voltage source represents the **barrier potential** that must be exceeded by the bias voltage before the diode will conduct and **is not an active source of voltage**.

- When conducting, a voltage drop of 0.7 V appears across the diode.
- When the diode is **reverse-biased**, it is equivalent to an open switch just as in the ideal model.

Since the **barrier potential** is included, the diode is assumed to have a voltage across it when forward-biased, as indicated by the portion of the curve to the right of the origin.

$$V_F = 0.7 V$$


The **forward current** is determined as follows by first applying Kirchhoff's voltage law

$$I_F = \frac{V_{BIAS} - V_F}{R_{LIMIT}}$$


The diode is assumed to have **zero reverse current**, as indicated by the portion of the curve on the negative horizontal axis.

$$I_R = 0 A$$



$$V_R = V_{BIAS}$$

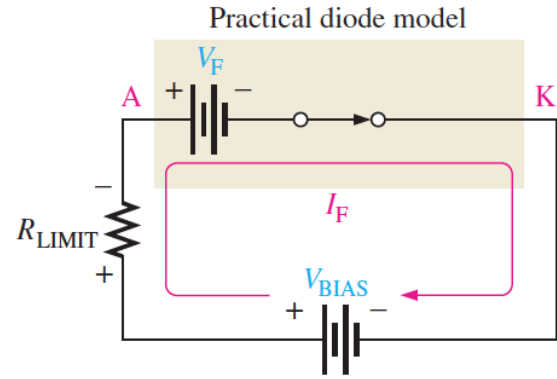

Forward bias

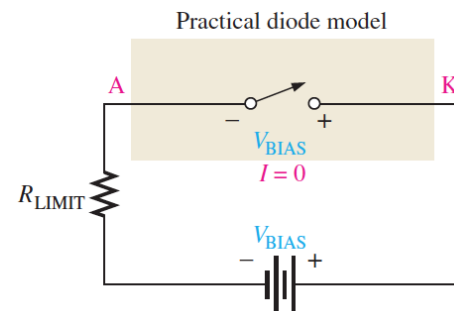


Reverse bias

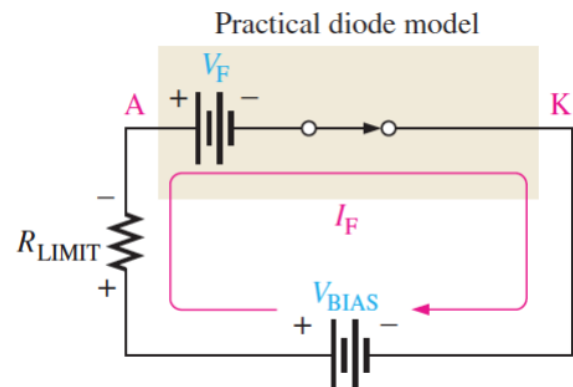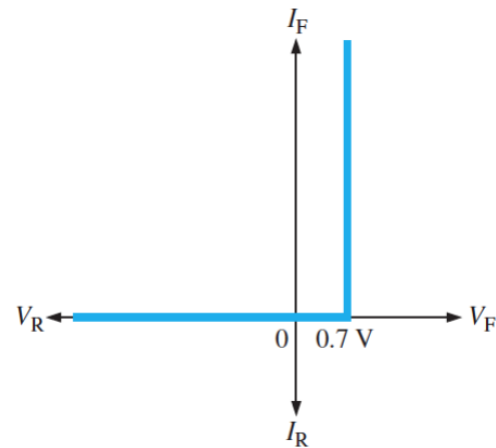


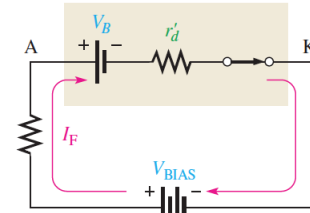6. The Complete Diode Model

When the diode is forward-biased, it acts as a closed switch in series with the equivalent barrier potential voltage (V_B) and the small forward dynamic resistance (r'_d).



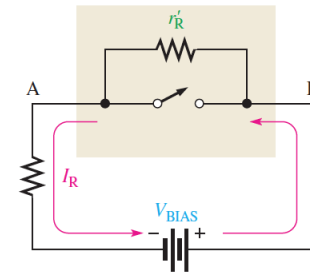
When the diode is reverse-biased, it acts as an open switch in parallel with the large internal reverse resistance (r'_R).




The barrier potential does not affect reverse bias, so it is not a factor.

The curve slopes because the voltage drop due to dynamic resistance increases as the current increases.

$$V_F = 0.7V + I_F r'_d$$

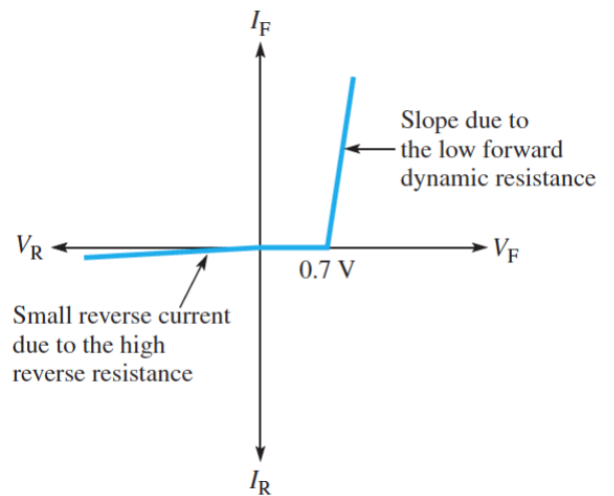

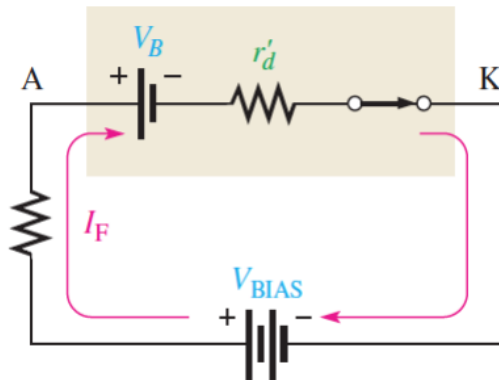The characteristic curve for the complete diode mode




$$I_F = \frac{V_{BIAS} - 0.7V}{R_{LIMIT} + r'_d}$$

a) Determine the **forward voltage** and **forward current** for the diode in Figure (a) for each of the diode models. Also find the voltage across the limiting resistor in each case. Assume $r'_d = 10 \Omega$ at the determined value of forward current.

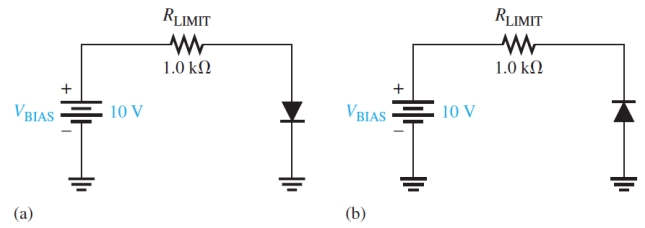b) Determine the **reverse voltage** and **reverse current** for the diode in Figure (b) for each of the diode models. Also find the voltage

across the limiting resistor in each case. Assume $I_R = 1 \mu A$.



Solution:

(a) - Ideal Model

$V_F = 0 V$

$$I_F = \frac{V_{BIAS}}{R_{LIMIT}} = \frac{10 V}{1.0 k\Omega} = 10 mA$$

$$V_{R_{LIMIT}} = I_F R_{LIMIT} = (10 mA)(1.0 k\Omega) = 10 V$$

- Practical Model

$V_F = 0.7 V$

$$I_F = \frac{V_{BIAS} - V_F}{R_{LIMIT}} = \frac{10 V - 0.7 V}{1.0 k\Omega} = \frac{9.3 V}{1.0 k\Omega} = 9.3 mA$$



$$V_{R_{LIMIT}} = I_F R_{LIMIT} = (9.3 mA)(1.0 k\Omega) = 9.3 V$$

- Complete Model

$$I_F = \frac{V_{BIAS} - 0.7 V}{R_{LIMIT} + r'_d} = \frac{10 V - 0.7 V}{1.0 k\Omega + 10 \Omega} = \frac{9.3 V}{1010 \Omega} = 9.21 mA$$

$$V_F = 0.7 V + I_F r'_d = 0.7 V + (9.21 mA)(10 \Omega) = 792 mV$$
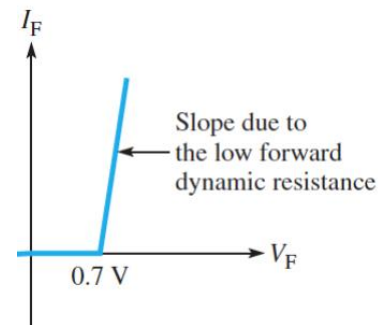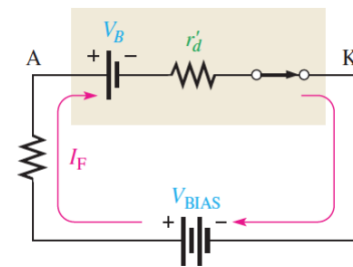
$$V_{R_{LIMIT}} = I_F R_{LIMIT} = (9.21 mA)(1.0 k\Omega) = 9.21 V$$



$V_R = V_{BIAS} = 10 V$

$V_{R_{LIMIT}} = 0 V$

(b) - Ideal Model


$I_R = 0 A$

- Practical Model

$$I_R = 0 \text{ A}$$

$$V_R = V_{BIAS} = 10 \text{ V}$$

$$V_{RLIMIT} = 0 \text{ V}$$

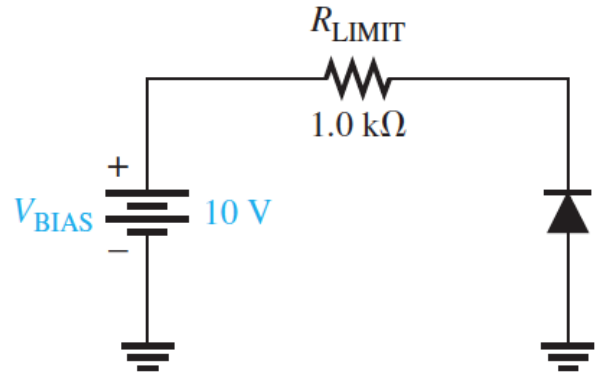


(b)

- Complete Model

$$I_R = 1 \mu\text{A}$$


$$V_{RLIMIT} = I_R R_{LIMIT} = (1 \mu\text{A})(1.0 \text{ k}\Omega) = 1 \text{ mV}$$
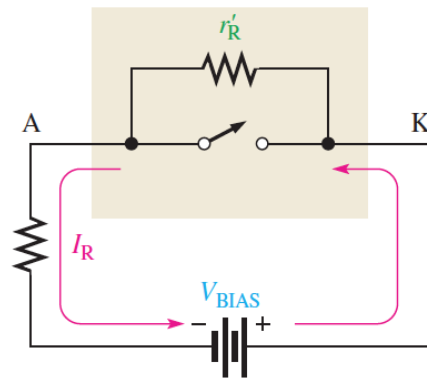
$$V_R = V_{BIAS} - V_{RLIMIT} = 10 \text{ V} - 1 \text{ mV} = 9.999 \text{ V}$$



Exercise

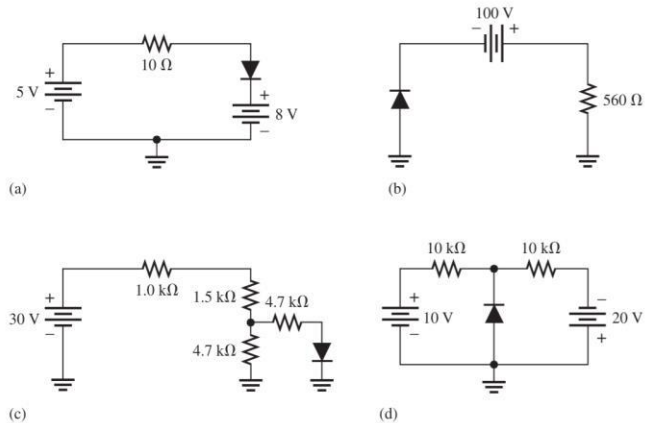1. Determine whether each silicon diode in Figure is forward-biased or reverse-biased.
2. Determine the voltage across each diode in Figure, assuming the **practical model**.
3. Determine the voltage across each diode in Figure, assuming an **ideal diode**.
4. Determine the voltage across each diode in Figure, using the **complete diode model** with $r'_d = 10 \Omega$, $r'_R = 100 \text{ M}\Omega$.



7. *Problem to solve by yourself*

In your textbook Solve Problems under section 1.9

36 to 38 Page 53

4-6