

كلية الهندسة	الكلية
قسم الهندسة الكهربائية	القسم
Fundamentals of Electronics I	المادة باللغة الانجليزية
أسس الإلكترونيك ١	المادة باللغة العربية
الثانية	المرحلة الدراسية
حامد ردام حسين	اسم التدريسي
SEMICONDUCTOR DIODES	عنوان المحاضرة باللغة الانجليزية
ثنائيات أشباه الموصلات	عنوان المحاضرة باللغة العربية
8	رقم المحاضرة
Electronic Devices and Circuit Theory 11 <sup>th</sup> Edition by Robert L. Boylestad, Louis Nashelsky	المصادر والمراجع
Electronic Devices 9th Edition by Thomas L. Floyd	

## Lecture 6: Load Line Analysis

### 1. Diode Applications


- Load-Line Analysis.
- Series Diode Configuration.
- Series-Parallel Configuration.
- Half-Wave Rectification.
- Full-Wave Rectification.
- Clippers.
- Clampers.
- Networks with a dc and ac Source.
- Zener Diodes.
- Voltage-Multiplier Circuits.

### 2. Unit Two Objectives

- Understand the concept of **Load-Line analysis** and how it is applied to diode networks.
- Become familiar with the use of **equivalent circuits** to analyze **series** and **series-parallel diode** networks.
- Understand the process of **rectification** to establish a dc level from a sinusoidal ac input.
- Be able to predict the output response of **clipper** and **clamper** diode configuration.
- Became familiar with the analysis, and the range of applications for **Zener** diode.

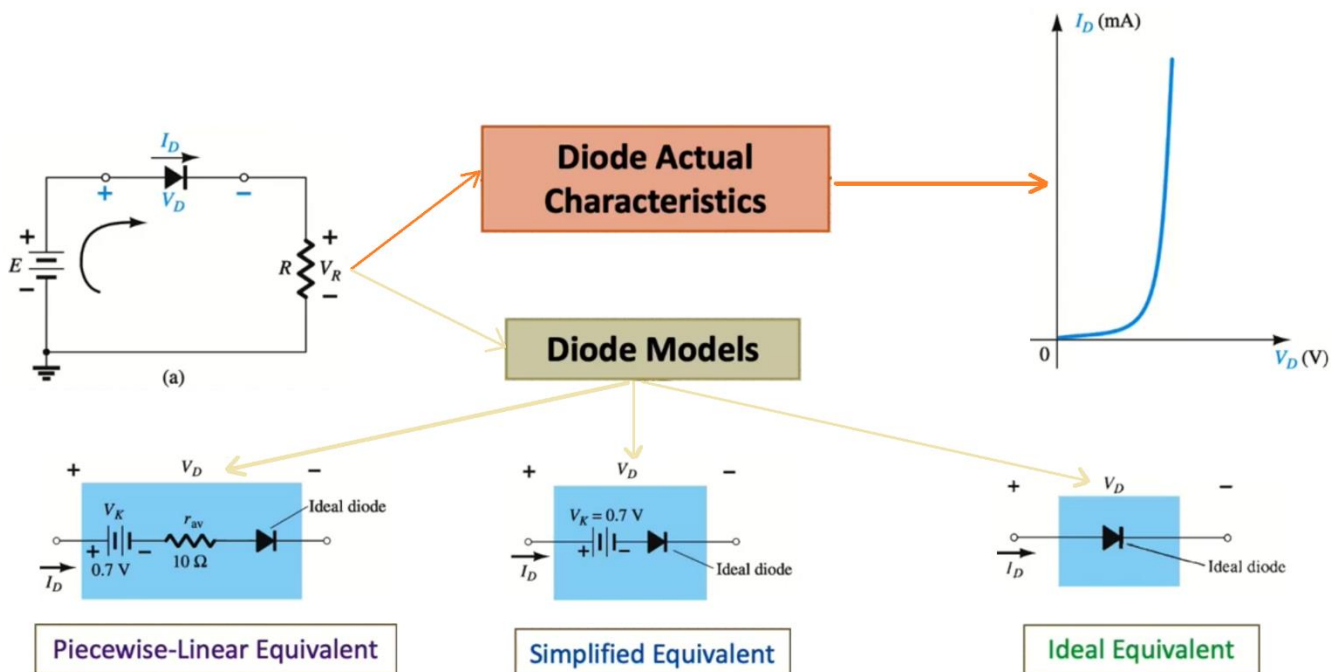
### 3. Analysis of a Diode Circuit

- Finding the **current** and **voltage** levels that will satisfy **both** the **characteristics** of the diode and the chosen **network parameters**.


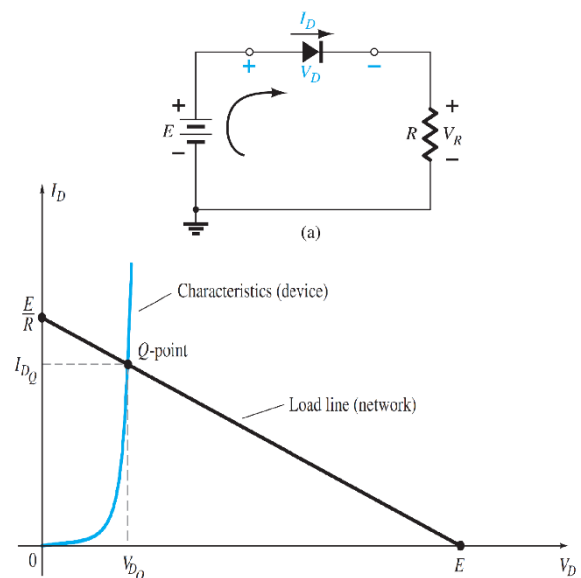
### 4. Drawing the Load Line


- The **straight line intersect** with the **diode characteristic curve** is called a **load line** because the **intersection** on the vertical axis is defined by the applied **load R**. The analysis called **Load-Line analysis**.
- The **intersection** of the two curves will define the solution for the network and define the **current and voltage levels** for the network.



- Let's see how we draw the **load line** of the **forward biased diode** on its **characteristic curve**.
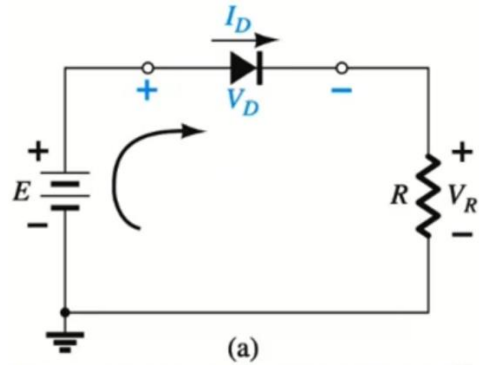
## 5. Load Line Analysis

- The diode in the circuit is in the forward-bias state.



- A Voltage across the diode is **0.7 V**.

- The intersection of the load line on the characteristics can be determined by applying Kirchhoff's voltage law (KVL):

$$-E + V_D + V_R = 0$$

$$E = V_D + I_D R$$

The two variables of  $V_D$  and  $I_D$ , are the same as the diode axis variables of characteristics curve.

- The intersections of the Load line on the characteristics can be determined from the equation  $E = V_D + I_D R$


If we set  $V_D = 0 V$  and solve for  $I_D$

$$I_D = \frac{E}{R} \Big|_{V_D=0 V}$$


If we set  $I_D = 0 A$  and solve for  $V_D$

$$V_D = E \Big|_{I_D=0 A}$$

Diode Circuit

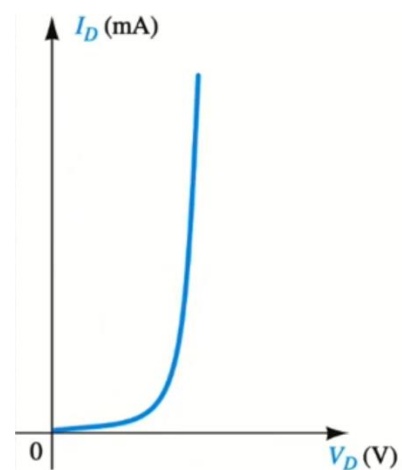

Diode characteristics

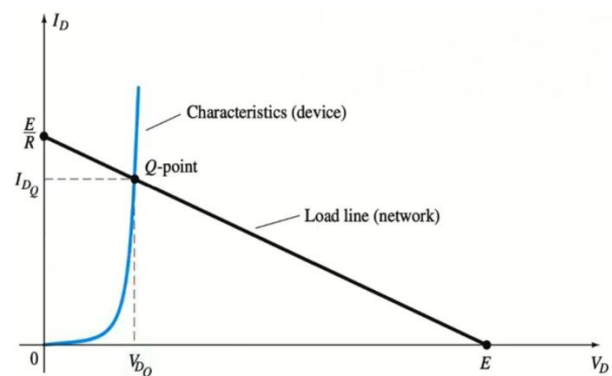


Change the level of the load ( $R$ ), the intersection on the vertical axis will change. The result will be a change in the slope of the Load line and a different point of intersection between the load line and the device characteristics.

## 6. Operation Point (Q Point)

The **point of intersection** between the Load line and the characteristic curve is the **point of operation of the diode** and is called the **quiescent point (Q-point)**, which is  $V_{DQ}$  and  $I_{DQ}$ .

$I_{DQ}$  by drawing a horizontal line from the point of intersection to the Y-axis.

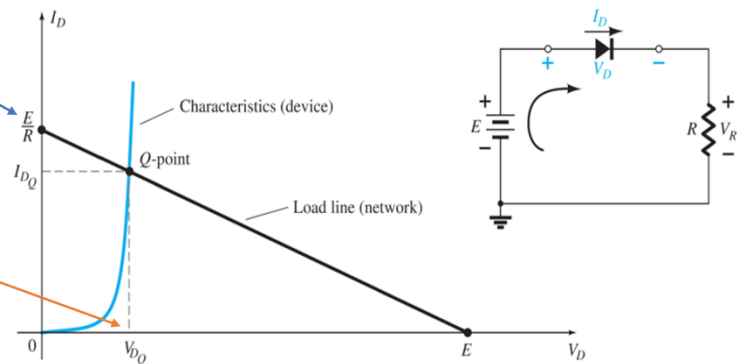
$V_{DQ}$  by drawing a vertical line from the point of intersection to the X-axis.



### Example 2.1

For the series diode configuration of Figure (a), employing the diode characteristics of Figure (b) determine:

- $V_{DQ}$  and  $I_{DQ}$
- $V_R$

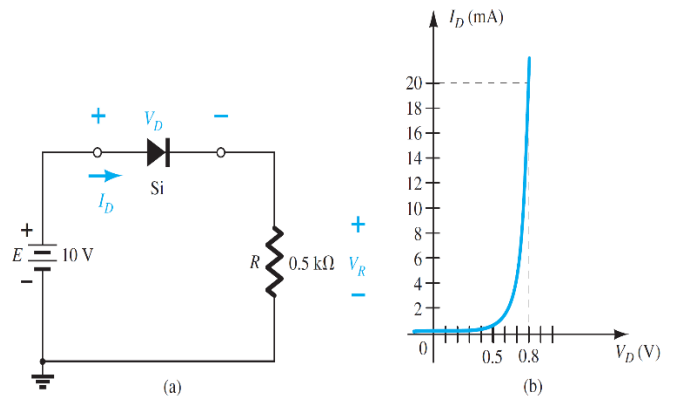

### Solution:

- $V_{DQ}$  and  $I_{DQ}$  We need to draw the load line

$$I_D = \frac{E}{R} \Big|_{V_D=0V} = \frac{10V}{0.5k\Omega} = 20\text{ mA}$$


$$V_D = E \Big|_{I_D=0A} = 10V$$

The intersection between the load line and the characteristic curve defines the Q-point as

$$V_{DQ} \cong 0.78V$$

$$I_{DQ} \cong 18.5\text{ mA}$$

- $V_R = E - V_D = 10V - 0.78V = 9.22V$

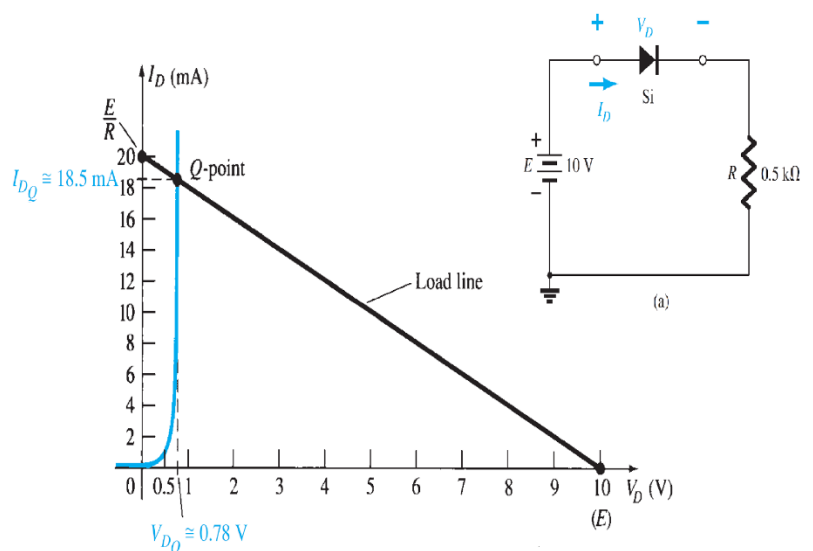

Note: The **load line is determined by the applied network**, whereas the characteristics are defined by the chosen device.

## 7. Working with equivalent network (Diode models)

We will replace the diode with dc resistance.

$$R_{DC} = V_D / I_D$$


Using the Q-point values (0.78 V, 18.5 mA), the dc resistance for Example. 2.1 is:

$$R_D = \frac{V_{DQ}}{I_{DQ}} = \frac{0.78 \text{ V}}{18.5 \text{ mA}} = 42.16 \Omega$$

The current and voltage are:

$$I_D = \frac{E}{R_D + R} = \frac{10 \text{ V}}{42.16 \Omega + 500 \Omega} = \frac{10 \text{ V}}{542.16 \Omega} \cong 18.5 \text{ mA}$$
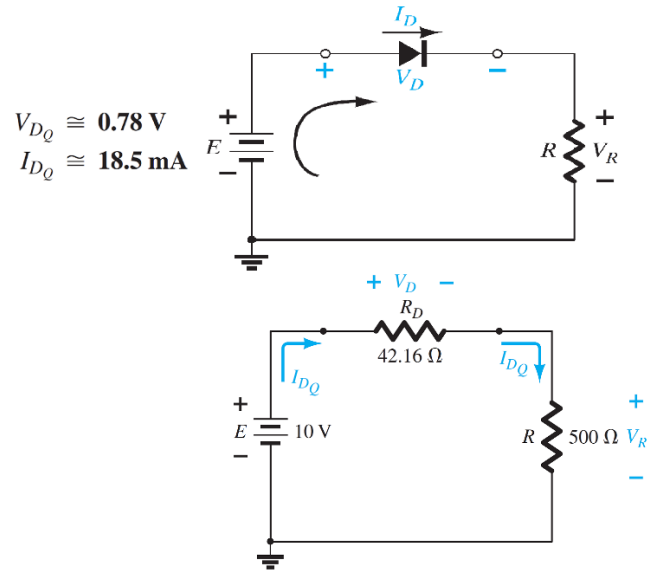
$$V_R = \frac{R \cdot E}{R_D + R} = \frac{(500 \Omega)(10 \text{ V})}{42.16 \Omega + 500 \Omega} = 9.22 \text{ V}$$



Once a dc Q-point has been determined the diode can be replaced by its dc resistance equivalent.

### Example 2.2:

Repeat example 2.1 using the approximate equivalent model for the Si diode.

**Solution:** The Load line is redrawn as shown, with the same intersections as defined in Example 2.1. The resulting in Q-point is:

$$V_{DQ} = 0.7 \text{ V}$$


&

$$I_{DQ} = 18.5 \text{ mA}$$

The dc resistance of the Q-point is:

$$R_D = \frac{V_{DQ}}{I_{DQ}} = \frac{0.7 \text{ V}}{18.5 \text{ mA}} = 37.84 \Omega$$

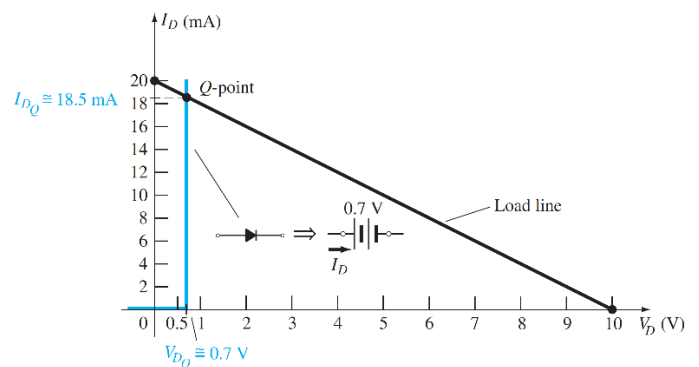Which is still relatively close to that obtained for the full characteristics.



### Example 2.3

Repeat example 2.1 using the ideal diode model.


**Solution:** The Load line is the same as in Example 2.1, but the ideal characteristics now intersect the Load line on the vertical axis.

The Q-point is therefore defined by:

$$V_{DQ} = 0 V \text{ \& } I_{DQ} = 20 mA$$

The results are sufficient different from the solution of example 2.1.
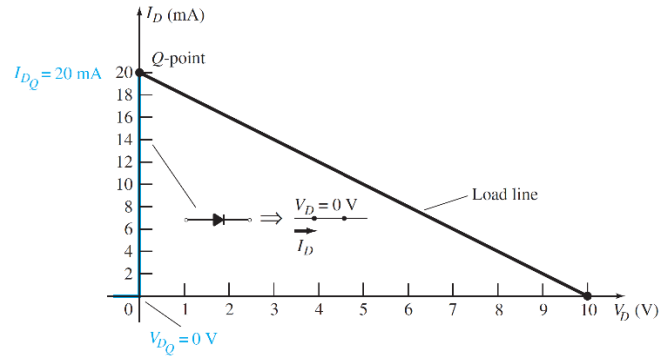
$$R_D = \frac{V_{DQ}}{I_{DQ}} = \frac{0 V}{20 mA} = 0 \Omega$$



**Note:** Use of the **ideal diode model** should be reserved for those situations where the applied voltages are considerably larger than the threshold voltage  $V_k$  .

## **8. Problems to Solve by Yourself**

**In your textbook solve problems under  
sections 2.2 Load-Line Analysis**

1, 2, 3 and 4

Pages 119 and 120