

Ministry of Higher Education and Scientific Research

University of Anbar

College of Computer Science and Information
Technology

Department of Computer Science

Logic Design – Lecture 4

Karnaugh Maps (K-Maps) and Logic Simplification

Instructor: Mohammed Shehab Hamad

1. Introduction to K-Maps

- Karnaugh Maps (K-Maps) are a method of simplifying Boolean algebra expressions. They provide a visual means of grouping terms to eliminate variables and reduce expressions to their simplest form.
- K-Maps were introduced by Maurice Karnaugh in 1953 to improve the simplification process of Boolean functions.
- Each K-Map corresponds to a truth table, and it provides a graphical method of representing logic functions.
- K-Maps are more efficient than algebraic simplification for functions with up to 6 variables.

2. K-Map Structures and Notation

- A 2-variable K-Map contains 4 cells, each representing one minterm.
- A 3-variable K-Map contains 8 cells. A 4-variable K-Map contains 16 cells.
- Each cell corresponds to a unique combination of variable states (e.g., $A'B$, AB' , etc.).
- Gray code is used in K-Maps to ensure only one bit changes between adjacent cells.

3. Simplification Rules

- Groups must contain 1, 2, 4, 8, etc. (powers of 2) cells.
- Groups must be rectangular and can wrap around the edges.
- Larger groups result in simpler expressions.

- Overlapping groups are allowed and often necessary for optimal simplification.
- Each 1 in the K-Map must be included in at least one group.

4. Examples of Simplification

- Example 1: Simplify $F(A, B) = (1, 3)$
- K-Map: $[0, 1; 0, 1]$ Group (1, 3) $F = B$
- Example 2: $F(A, B, C) = (1, 2, 3, 5, 7)$
- Group adjacent 1s: (1, 3), (5, 7), (3, 7) $F = B'C + AC$
- Example 3: 4-variable function with (0,1,2,5,6,7,8,9,10,14)
- Multiple possible groupings Choose largest rectangles to reduce the function
- Example 4: Simplify $F(A,B,C,D) = (0,1,2,5,6,7,8,9)$
- Step 1: Construct the 4-variable K-Map with 16 cells.
- Step 2: Fill the cells with 1s at specified minterms.
- Step 3: Group adjacent 1s into largest possible rectangles.
- Step 4: Derive simplified expression.
- Result: $F = B'D' + AC$
- K-Map Table (Text Representation):
- CD | 00 | 01 | 11 | 10 |
- AB -----
- 00 | 1 | 1 | 0 | 1 |

- 01 | 1 | 1 | 0 | 0 |
- 11 | 1 | 1 | 0 | 0 |
- 10 | 0 | 0 | 0 | 0 |

5. Don ' t Care Conditions

- Don't care conditions are outputs where the function can be either 0 or 1 without affecting functionality.
- They are marked with 'X' in K-Maps.
- Used to create larger groups when simplifying expressions.
- Example: $F(A,B,C) = (1,3,7)$, $d(A,B,C) = (2,6)$ include 2 and 6 in groups if beneficial

6. POS (Product of Sums) Simplification with K-Maps

- K-Maps can also be used to simplify expressions in Product of Sums (POS) form.
- Instead of grouping 1s, we group 0s and derive the maxterms.
- Example: $F = M(0,2,5)$ K-Map shows zeros in these positions derive sum terms from ungrouped areas

7. Common Mistakes

- Not using wrap-around groups.
- Making groups that are not powers of 2.
- Overlooking don ' t care terms that could simplify the expression further.

- Incorrectly assigning variable combinations to K-Map cells.

8. Practice Exercises

- Simplify: $F(A,B,C,D) = (0,2,5,6,8,10,13,15)$
- Simplify: $F(W,X,Y,Z) = (1,3,7,11,15)$ with $d(W,X,Y,Z) = (0,2,5)$
- Simplify: $F = M(0,1,3,7,8,9)$
- Design a logic circuit from the simplified expression of $F = (1,2,3,5,7)$
- Draw a 4-variable K-Map and show all possible groupings for $F = (0,1,2,5,6,7,8,9)$
- Design a combinational logic circuit for a vending machine that accepts A and B inputs (coins) and outputs 1 if the total equals 10 cents.
- Draw the K-Map for this system and simplify the logic.
- Draw the truth table and K-Map for a 3-input majority function (outputs 1 if at least 2 inputs are 1).
- Construct the 4-variable K-Map for a logic function where the output is 1 only when exactly two inputs are true.
- Challenge: Find the minimal expression using K-Map for $F(W,X,Y,Z) = (0,1,2,6,8,10,12,14)$ with don't cares at $(3,11)$.

9. Homework Assignment

- 1. Use K-Maps to simplify the following Boolean expressions:
 - a. $F(A,B,C) = (0,1,3,5,7)$

- b. $F(W,X,Y,Z) = (1,2,5,7,9,11,13)$
- 2. Identify the optimal groupings in a 4-variable K-Map for $F = (0,2,3,8,10,11,14,15)$
- 3. Convert the following truth table into a simplified Boolean expression using a K-Map.
- 4. Draw the logic diagram for the simplified result of $F(A,B,C,D) = (1,3,7,11,15)$

10. Summary

- K-Maps are a visual tool for simplifying logic expressions.
- Grouping 1s (or 0s for POS) in power-of-2 rectangles minimizes variables in the result.
- Don't care conditions can help further reduce logic expressions.
- K-Maps reduce errors and simplify circuit design for up to 4–6 variables effectively.

12. In-Class Discussion Questions

- 1. Why are overlapping groups allowed in K-Map simplification?
- 2. How does Gray code ordering help in the grouping process?
- 3. What would happen if we group non-adjacent 1s? Why is that invalid?
- 4. How can don't care conditions change the final simplified expression?
- 5. Why is grouping more than the minimum number of 1s often beneficial?

11. References

- M. Morris Mano, Digital Design, Pearson Education, 5th Edition.
- Ronald J. Tocci, Digital Systems: Principles and Applications, 11th Edition.
- Floyd, Digital Fundamentals, Pearson, 10th Edition.