

زكاة التبعة العجايب والبعث العليمي



جامعة الانبار كلية علوم الحاسوب وتكنولوجيا المعلومات قسم علوم الحاسبات

Department	علوم الحاسبات	القسم:
Subject Name:	Logic Design	أسم المادة :
Year of Study:	2025-2024	السنة الدراسية:
Course:	الكورس الاول	الكورس:
Title and No of lecture:	Lecture 6: Boolean algebra I	عنوان ورقم المحاضرة:
Instructor Name:	د. مصطفى معد حمدي	أسم التدريسي:
السنة : 2025-2024	اسم المادة: التصميم المنطقي	أستاذ المادة: د. مصطفى معد حمدي

LECTURE SIX

BOOLEAN ALGEBRA I

Objectives:-

1. Binary operators and their representations.
2. Relationships between Boolean expressions, Truth tables and Logic circuits.
3. Logic gates' postulates, laws and properties.

1. Binary operators and their representations

- *Boolean algebra* is the basic mathematics needed for logic design of digital systems; Boolean algebra uses *Boolean (logical) variables with two values (0 or 1)*.


"Two-valued Boolean algebra"

Basic operations:

- The basic operations of Boolean algebra are **AND**, **OR**, and **NOT** (*complement*).
- a) **NOT operation (NOT Gate):-**

$$\bar{1} = 0; \bar{0} = 1$$

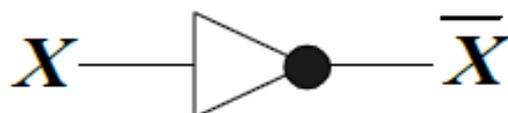- The **not** operator is also called the *complement* or the *inverse*:
- \bar{x} is the complement of x .
- Output is *opposite* of input.
- **Truth table**: truth table describes inputs and outputs in terms of 1_2 and 0_2 rather physical (voltage) levels.



Not gate representation

Truth table:


Input x	Output \bar{x}
0	1
1	0

1 - high
0 - low

b) AND operation (*AND gate*).


- The output is **1** only if all inputs are **1**, if any of the input is **0**, then the output is **0**.
- The truth table of *AND gate* (2-inputs, 1-output) as the following:

Inputs		Output
<i>A</i>	<i>B</i>	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

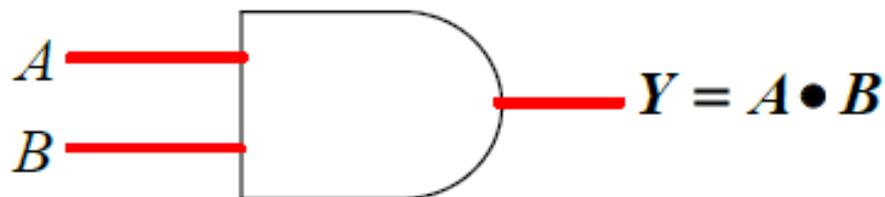

The AND operation is referred to as logical multiplication

c) OR operation (**OR gate**)

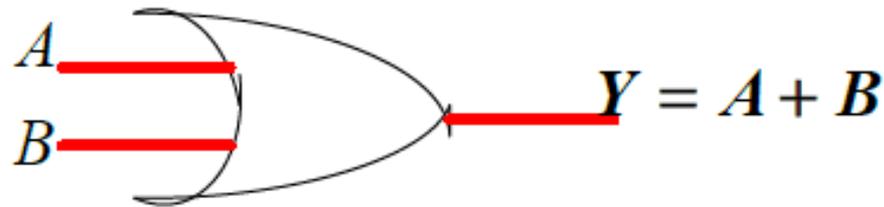


*The output is 1 if
A is 1 or if B is 1*

➤ The truth table of **OR** gate (2-inputs, 1-output) as the following:

Inputs		Output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

OR operation is sometimes referred to as "inclusive OR" or logical addition.


d) **NAND gate: (Not AND gate)**

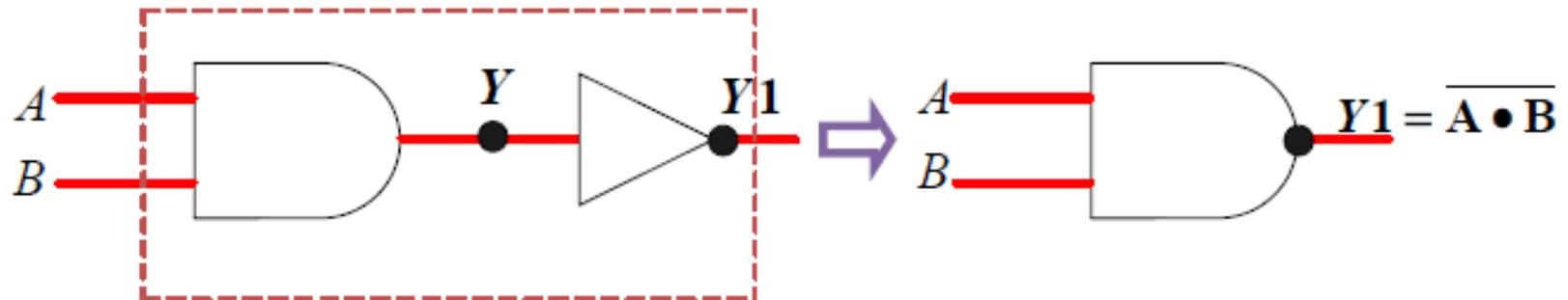

➤ The truth table of **NAND** gate (2-inputs, 1-output) as the following:

inputs		outputs	
A	B	$Y = A \cdot B$	$Y1 = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


e) **NOR gate (Not OR gate):**

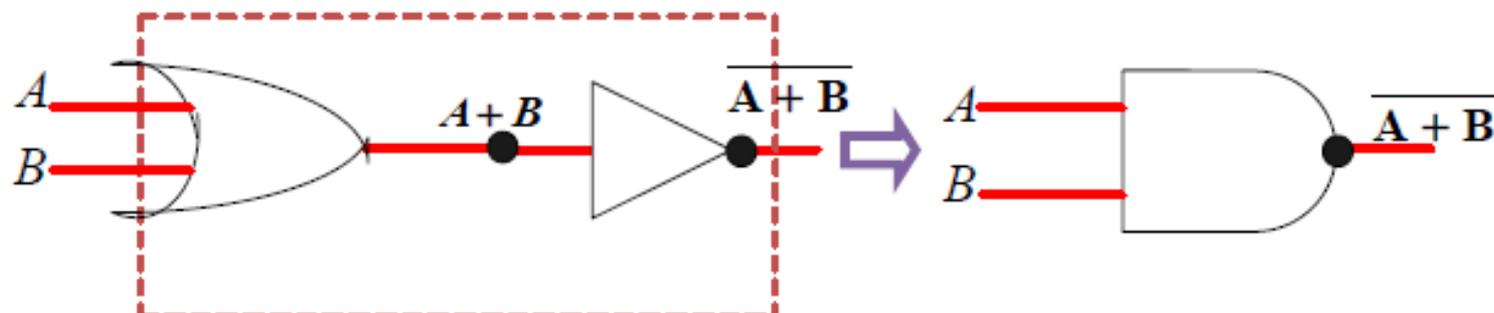

The truth table of **NOR** gate (2-inputs, 1-output) as the following:

inputs		outputs	
A	B	$A + B$	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

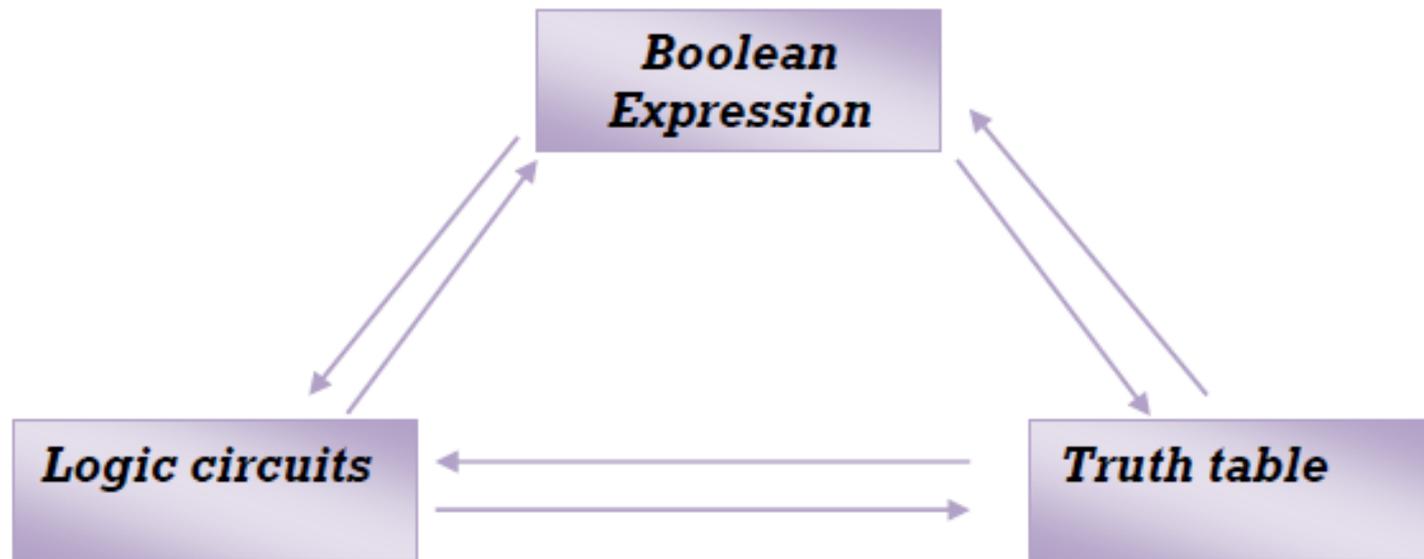2. Relationships between Boolean expression, truth tables and logic circuits




➤ If one is given, we can get the other.

To draw a circuit from a Boolean expression:

- ✓ From the left, make an *input line* for each variable.
- ✓ Next, put a **Not** gate in for each variable, that appears negated in the expression.
- ✓ Still working, from left to right.


Example 1:- $Z = A\bar{B}$

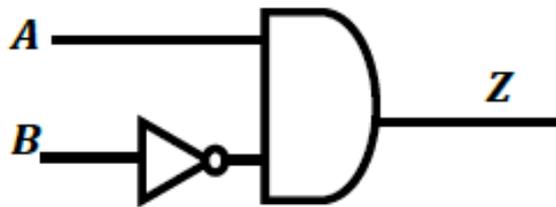

Precedence of operators:

1. Parenthesis
2. NOT
3. AND
4. OR

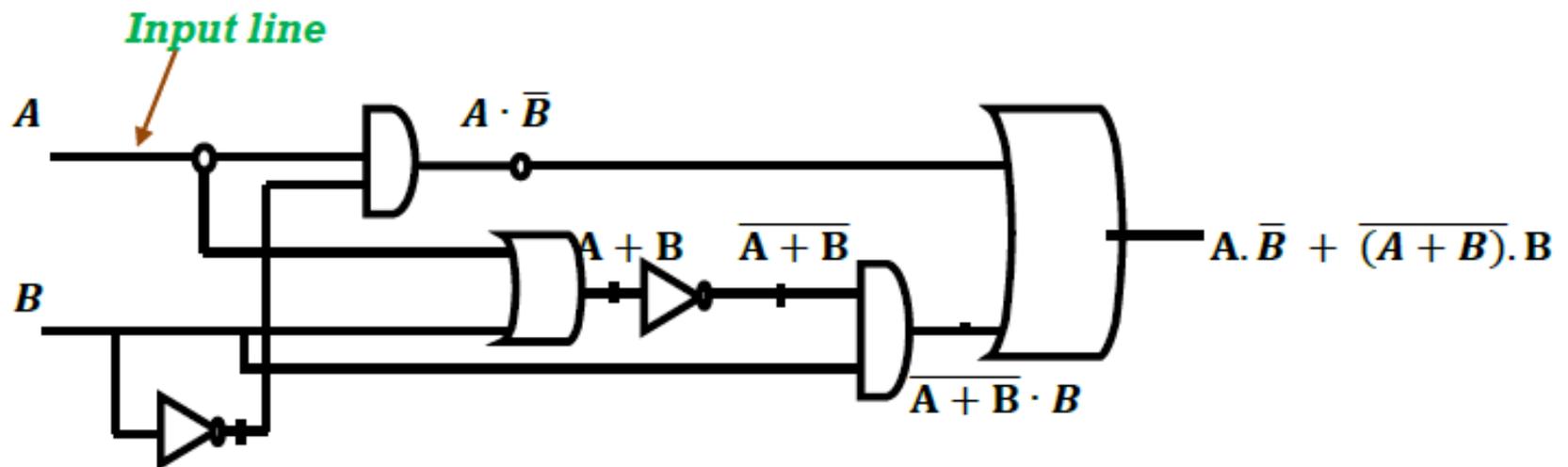Example 2:- $A\bar{B} + \overline{(A+B)} \cdot B$



3. Logic gate's postulates, laws and properties

➤ Postulates are used to deduce the rules, theorems and properties.

a) Postulates of Boolean algebra

Postulate	For OR Gate	For AND Gate
<i>P1</i>	$A + 0 = A$	$A \cdot 1 = A$
<i>P2</i>	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
<i>P3</i>	$A + B = B + A$	$A \cdot B = B \cdot A$
<i>P4</i>	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + B \cdot C = (A + B) \cdot (A + C)$
 Duality principle		

➤ *Duality principle* states that every algebraic expression is deducible if *the operators and the identity elements are interchanged.*

Identity elements:

0 for or gate

1 for and gate

b) Boolean algebra theorems:

➤ There are six theorems of Boolean algebra:

Theorem	For OR Gate	For AND Gate
T1: <i>Idempotent laws</i>	$A + A = A$	$A \cdot A = A$
T2: <i>operations with 0 and 1</i>	$A + 1 = 1$	$A \cdot 0 = 0$
T3: <i>associative laws</i>	$A + (B + C) = (A + B) + C$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$
T4: <i>de Morgan laws (inversion law)</i>	$\overline{A + B} = \bar{A} \cdot \bar{B}$	$\overline{A \cdot B} = \bar{A} + \bar{B}$
T5: <i>Absorption laws</i>	$A + A \cdot B = A$	$A \cdot (A + B) = A$
T6: <i>involution law</i>	$\overline{\bar{A}} = A$	

- To *proof* these theorems and other logic expressions, we can use *two ways*:
[1] Truth table

Example 1: proof that $A + A \cdot B = A$

A	B	$A \cdot B$	$A + A \cdot B$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

Example 2: verify the de Morgan's laws using a truth table.

A	B	\bar{A}	\bar{B}	$A + B$	$\overline{A + B}$	$\bar{A} \cdot \bar{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$	
0	0	1	1	0	1	1	0	1	1	
0	1	1	0	1	0	0	0	1	1	
1	0	0	1	1	0	0	0	1	1	
1	1	0	0	1	0	0	1	0	0	
					$\overline{A + B} = \bar{A} \cdot \bar{B}$			$\overline{A \cdot B} = \bar{A} + \bar{B}$		

Some Details:


- The duality principle is formed by *replacing AND with OR, OR with AND, 0 with 1, 1 with 0, variables and complements are left unchanged.*
- de Morgan's laws Allow us to *convert between types of gates*; we can generalize them to n variables:

$$\overline{(x_1 + x_2 + x_3 + \dots + x_n)} = \overline{x_1} \cdot \overline{x_2} \cdot \overline{x_3} \cdot \dots \cdot \overline{x_n}$$

$$\overline{(x_1 x_2 x_3 \dots x_n)} = \overline{x_1} + \overline{x_2} + \overline{x_3} + \dots + \overline{x_n}$$

The left side

The right side

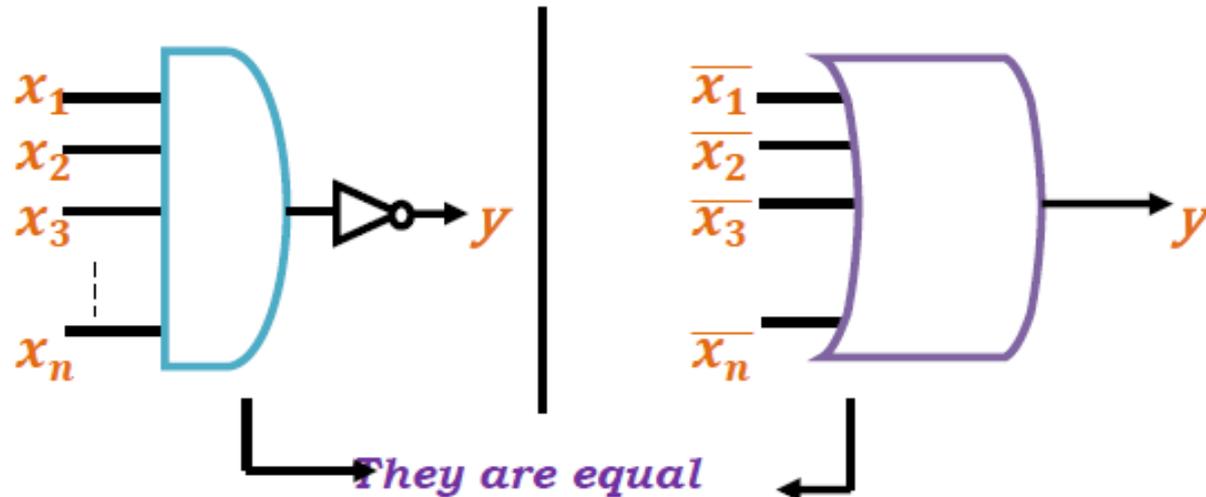

[2] Algebraically using basic theorems.

Example 1: verify that

a) $A + A \cdot B = A$

b) $A(A + B) = A$

Proof (a):

$$A + A \cdot B = A \cdot 1 + A \cdot B = A(1 + B) = A \cdot 1 = A$$

Proof (b):


$$A(A + B) = A \quad \text{by duality.}$$

Example 2

a) $(\overline{A}B + 0) \overline{E + 1} = 1$

b) $(\overline{A}B + 0) (\overline{A}B + 0) = 0$

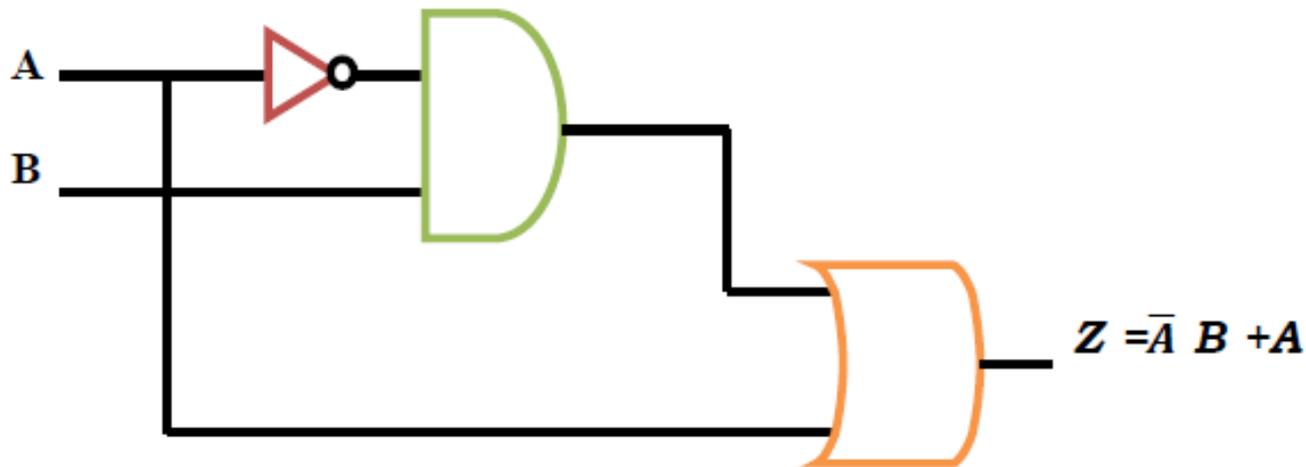c) An input A is inverted and applied to an **AND** gate. The other input is B . the output of the **AND** gate is applied to an **OR** gate. A is the second input to **OR** gate. *Draw the logic circuit and the truth table.*



<i>A</i>	<i>B</i>	<i>Z</i>
0	0	0
0	1	1
1	0	1
1	1	1

Truth table

d) Proof the following Boolean expression "*Theorems*".

a) $X + XY = X$

Proof:

$$x + xy = x \cdot 1 + xy = x(1 + y) = x \cdot 1 = x$$

b) $X(X + Y) = X$

Proof:

$$x(x + y) = x \cdot x + x \cdot y = x + xy = x(1 + y) = x \cdot 1 = x$$

c) $X\bar{Y} + Y = X + Y$

Proof:

$$x\bar{y} + y = y + x\bar{y} = (y + x)(y + \bar{y}) = (y + x) \cdot 1 = y + x$$

Homework: proof that

a) $(x + y)(x + \bar{y}) = x$

b) $(x + \bar{y})y = xy$