

# زكاة التبع العجايب والبعث العليمي



## جامعة الانبار كلية علوم الحاسوب وتكنولوجيا المعلومات قسم علوم الحاسبات

Department	علوم الحاسبات	القسم:
Subject Name:	Logic Design	أسم المادة :
Year of Study:	2025-2024	السنة الدراسية:
Course:	الكورس الاول	الكورس:
Title and No of lecture:	Lecture 8:Karnaugh Map Methods I	عنوان ورقم المحاضرة:
Instructor Name:	د. مصطفى معد حمدي	أسم التدريسي:

السنة : 2025-2024

اسم المادة: التصميم المنطقي

أستاذ المادة: د. مصطفى معد حمدي

# LECTURE EIGHT

## KARNAUGH MAP METHODS I

### Objectives:

1. Karnaugh Map definition.
2. Karnaugh map construction.
  - Two variables K-maps.
  - Three variables K-maps.
  - Four variables K-maps.
3. Summary

## 1) Karnaugh map definition


- The karnaugh map (k-map) is a *graphical tool* used to simplify (minimize) the logic functions, so that it can be implemented with minimum number of gates (minimum number of product terms and minimum number of literals).
- The K-map is used to *convert* a truth table to its corresponding logic circuit.

## 2) Karnaugh map construction

### • Two variables K-maps.

- A two- variable function has four possible minterms, we can rearrange these minterms into a karnaugh map:

$x$	$y$	Minterms
0	0	$\bar{x}\bar{y}$
0	1	$\bar{x}y$
1	0	$x\bar{y}$
1	1	$xy$

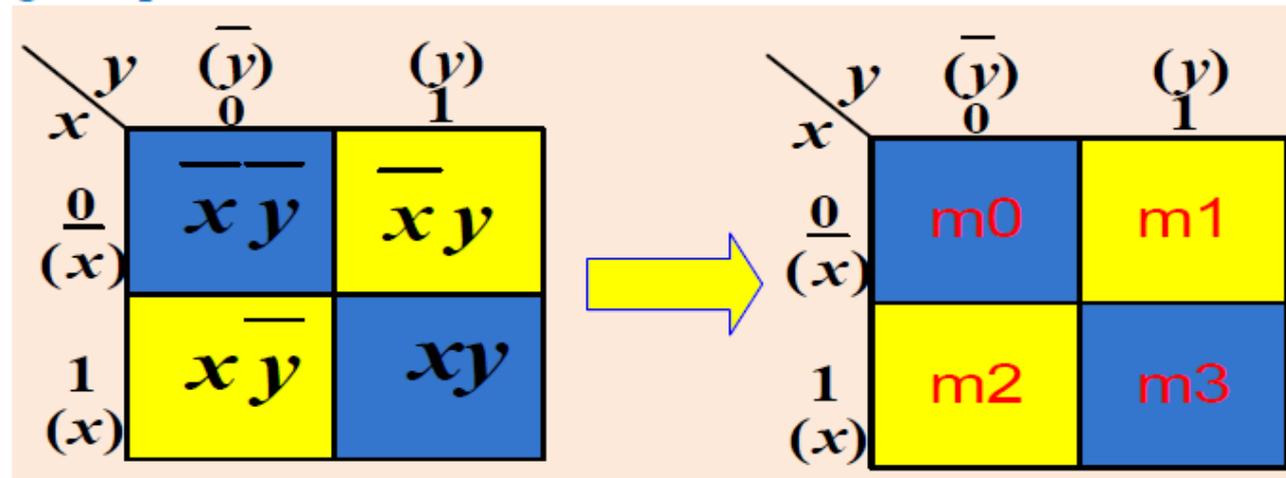

### Example:

$$F = xy + x\bar{y}$$

➤ The Karnaugh map for this function will be:

$x \backslash y$	$\bar{y}$ 0	$y$ 1
$\bar{x}$ 0	0	0
$x$ 1	1	1

➔  $F = xy + x\bar{y}$

Note: we can easily from the k-map see which *minterms contain common literal*:

- Minterms on the left and right sides contain  $\bar{y}$  and  $y$  respectively.

- Minterms in the top and bottom rows contain  $\bar{x}$  and  $x$  respectively.


$x \backslash y$	$\bar{y}$ 0	$y$ 1
$\bar{x}$ 0	$\bar{x}\bar{y}$	$\bar{x}y$
$x$ 1	$x\bar{y}$	$xy$

Note: each case in the truth table corresponds to a square in the K-map

- **Karnaugh map simplification:**

➤ The K-map squares labeled so that *horizontally adjacent* square differ only in one variable.


**Example 1:-** Imagine a two-variable sum of minterms, both of these minterms appear in the top row of a karnaugh map, which means that they both contain the literal  $\bar{x}$ .

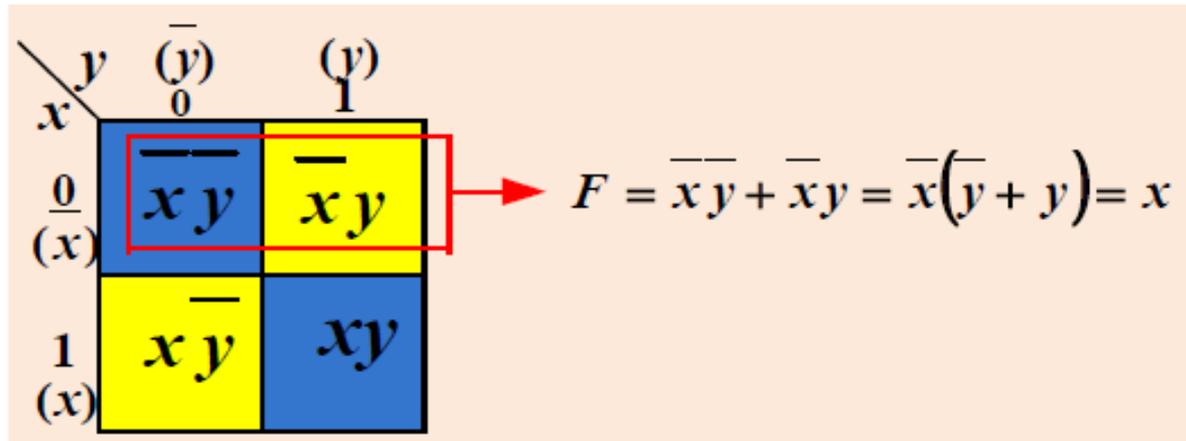

**Example 2:**  $f = \bar{x}y + xy$  -minimize it using K-map.

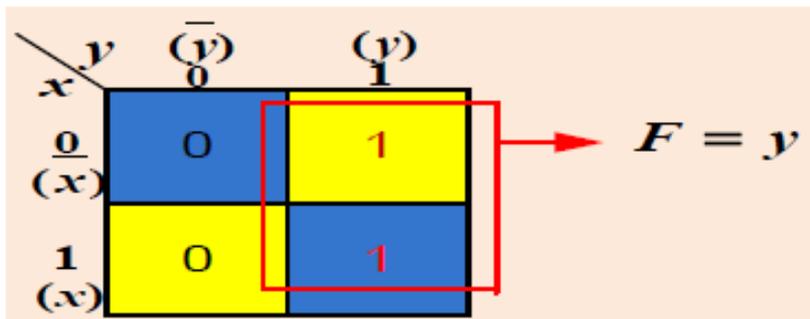**Solution:**


- Both minterms appear in the right- side where  $y$  is uncomplemented.
- Thus, we can reduce  $\bar{x}y + xy =$  just to  $y$ .



$$f = \bar{x}y + xy = y(x + \bar{x}) = y$$

**Example 3:**  $z = \bar{x}\bar{y} + \bar{x}y + xy$  -minimize it using K-map.

**Solution:**

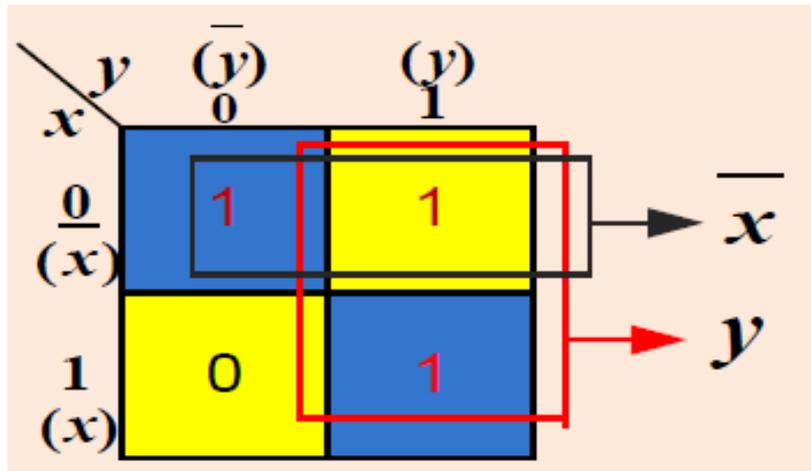

- We have  $\bar{x}\bar{y} + \bar{x}y$  in the top row, corresponding to  $\bar{x}$
- There's also  $\bar{x}y + xy$  in the right side corresponding to  $y$ .
- The result  $z = \bar{x} + y$ .


**Using algebraic simplification:**

$$z = \bar{x}\bar{y} + \bar{x}y + xy = \bar{x}(\bar{y} + y) + xy = \bar{x} + xy = (x + \bar{x})(\bar{x} + y) = \bar{x} + y$$


- **Three- variables K-map**

- For  $F(A, B, C)$  there are  $2^3 = 8$  minterms.
- *Representation* truth table using K-map

○ Different versions:

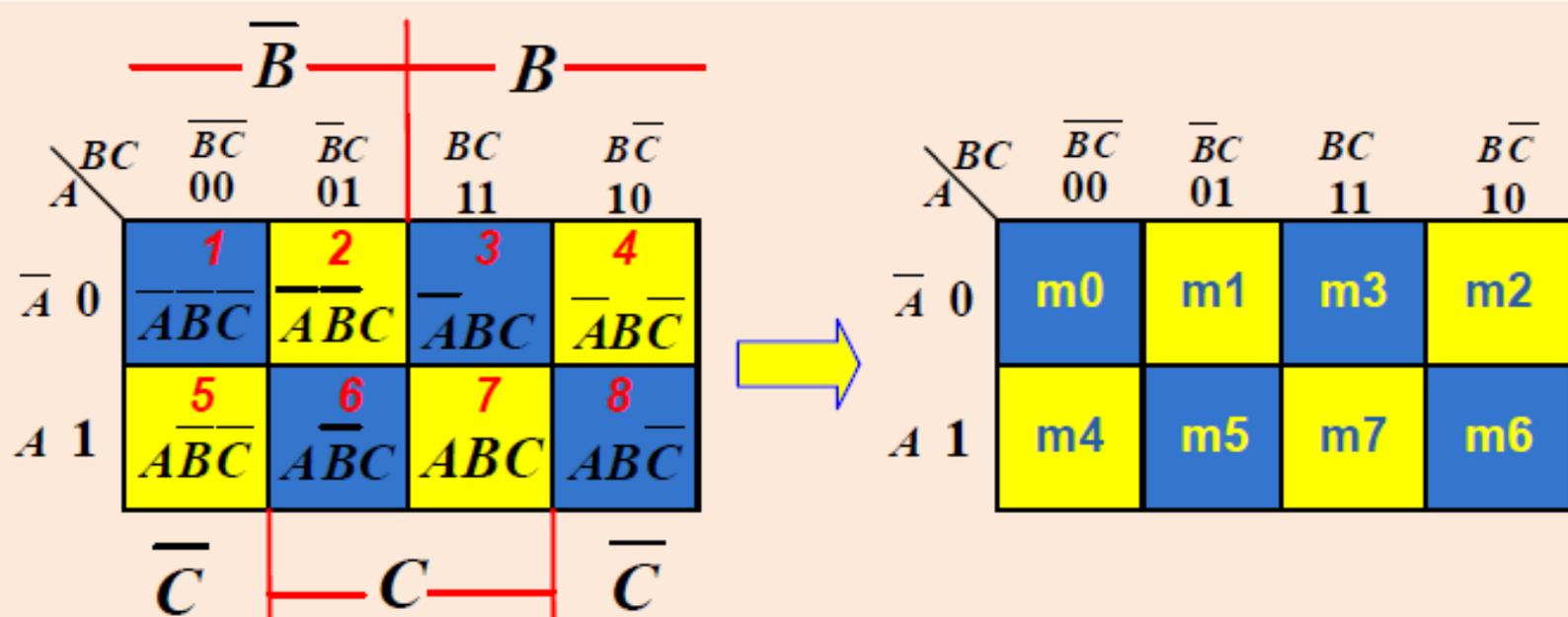

Or

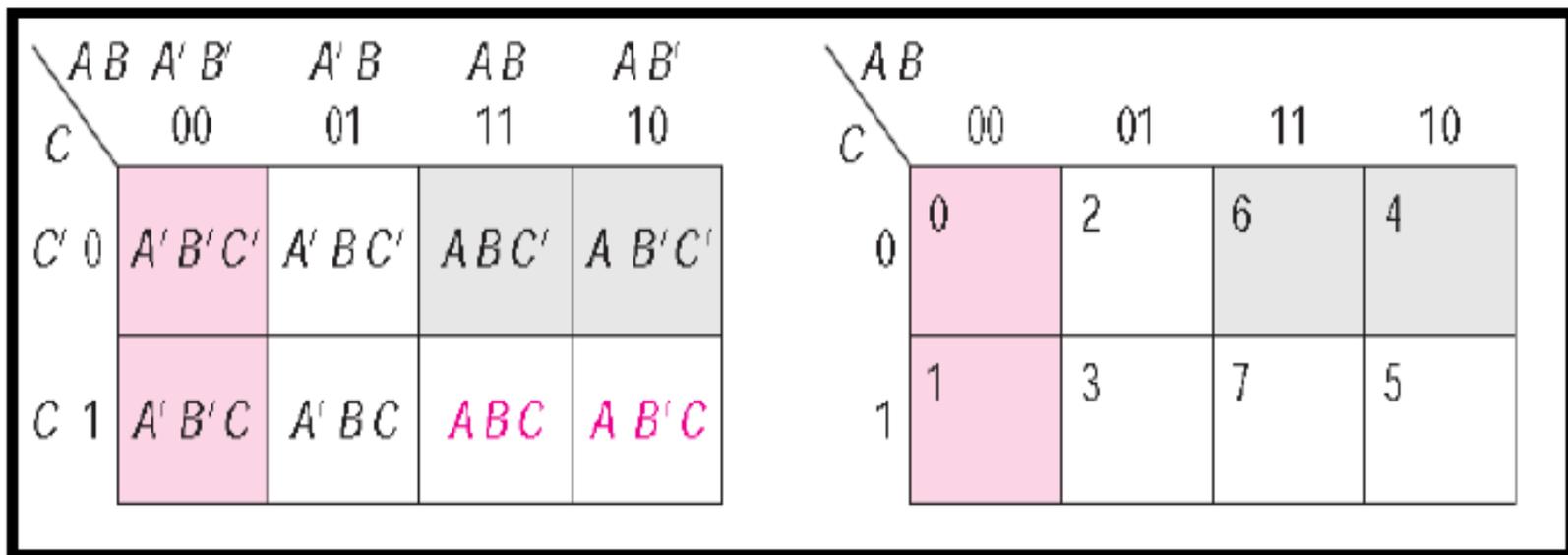

## Grouping (ordering, looping)

➤ The groups can be 2, 4, or 8 adjacent squares:

- ✓ **2 squares** → 1 variable can be canceled.
- ✓ **4 squares** → 2 variables can be canceled.
- ✓ **8 squares** → 3 variables can be canceled.


➤ **Examples:-**

Squares	Common Literal (s)
(1) and (2)	$\bar{A} \bar{B}$
(2) and (3)	$\bar{A} C$
(1) and (4)	$\bar{A} \bar{C}$
(1), (2), (5) and (6)	$\bar{B}$
(3), (4), (7) and (8)	$B$
(1), (2), (3) and (4)	$\bar{A}$
(5), (6), (7) and (8)	$A$
(1), (5), (4) and (8) (Wrapping case is also adjacent)	$\bar{C}$

- To *proof* the wrapping case (the last one in the table) algebraically, we can write:

$$\begin{aligned}
 F &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} B \bar{C} + A B \bar{C} \\
 &= \bar{C}(\bar{A} \bar{B} + A \bar{B} + \bar{A} B + AB) \\
 &= \bar{C}(\bar{B}(\bar{A} + A) + B(\bar{A} + A)) \\
 &= \bar{C}(\bar{B} + B) = \bar{C}
 \end{aligned}$$

- "*Adjacency*" includes wrapping around the left and right side.

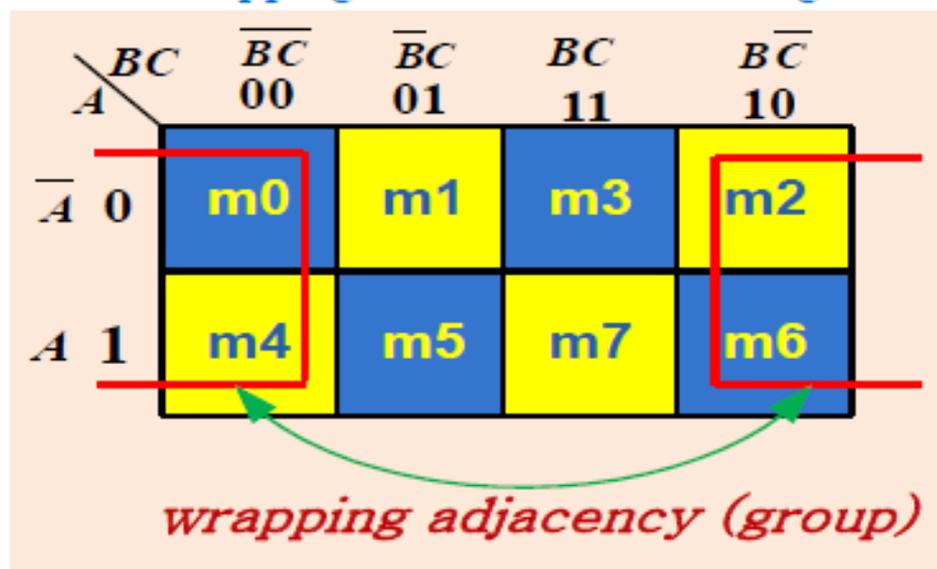

**Example 1:** Simplify the following logical function using K-map.

$$F(x, y, z) = xy + \bar{y}z + xz$$

**Solution:**

**Step 1:** the expression must be in a sum of minterms form, so we should convert it:(two ways to do that):

1. Using logical rules (algebraically).

$$\begin{aligned}
 F &= xy + \bar{y}z + xz \\
 &= xz(z + \bar{z}) + \bar{y}z(x + \bar{x}) + xz(y + \bar{y}) \\
 &= xyz + xy\bar{z} + x\bar{y}z + \bar{x}\bar{y}z + \cancel{xyz} + \cancel{x\bar{y}z} \\
 &= xyz + xy\bar{z} + x\bar{y}z + \bar{x}\bar{y}z \\
 &= m_1 + m_5 + m_6 + m_7
 \end{aligned}$$

2. Make the truth table and read the minterms.

$$F = xy + \bar{y}z + xz$$

inputs			Output	Terms replacement
x	y	z	$F(x,y,z)$	
0	0	0	0	
0	0	1	1	$\bar{y}z$
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	$xz$ and $\bar{y}z$
1	1	0	1	$xy$
1	1	1	1	$xy$ and $xz$

$$\begin{aligned}
 F(x,y,z) &= \bar{x}\bar{y}z + x\bar{y}z + xy\bar{z} + xyz \\
 &= m_1 + m_5 + m_6 + m_7
 \end{aligned}$$

**Step 2:** fill one's (for the minterms) in karnaugh map; zero's for other squares.

$x \backslash yz$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$\bar{y}z$        $xy$

**Step 3:** grouping (looping):

2 groups:

(m1) and (m5)

(m6) and (m7)

**Step 4:** simplify:

$$F = xy + \bar{y}z$$

➤ To **proof** the result:

$$\begin{aligned} F &= \bar{x}\bar{y}z + x\bar{y}z + xyz + xy\bar{z} \\ &= \bar{y}z(x + \bar{x}) + xy(z + \bar{z}) \\ &= \bar{y}z + xy \end{aligned}$$

### Grouping the minterms:-


- Grouping together all the  $1_s$  in the K-map.
  - Make rectangles of  $2^n$  (1, 2, 4, ...).
  - All the  $1_s$  in the map should be included in at least one rectangle.
  - *Do not* include any of the  $0_s$ .
  - Each group corresponds to one product term.
  - Make each rectangle *as large as possible*.
  - We can *overlap the rectangles*, if that makes them larger.

**Example 2:** Simplify the following logical function using K-map.

$$Z = AB + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C}$$

**Solution:**


$$Z = AB + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C}$$

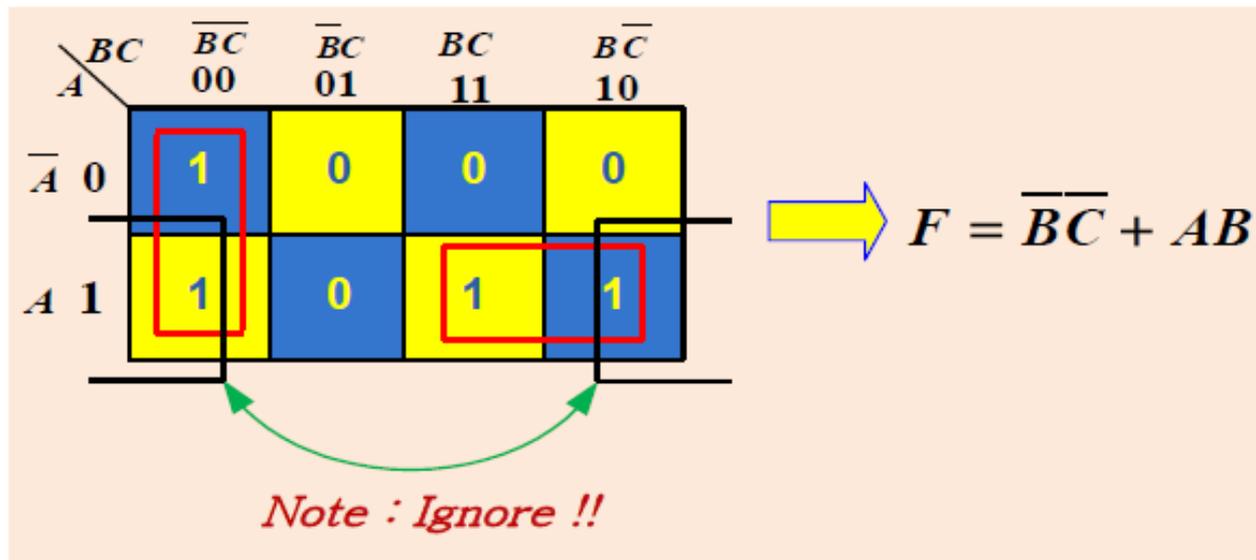

**Example 3:** Simplify the following logical function using K-map.

$$Z = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + A\overline{B}\overline{C} + ABC$$

**Solution:**

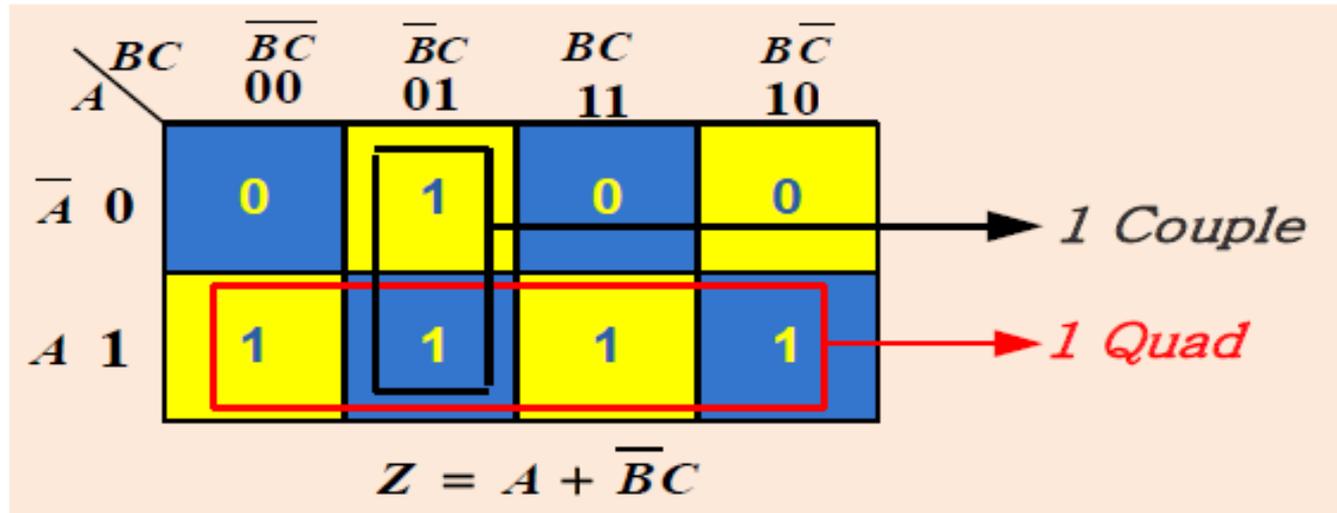

**Quad:**

$$\begin{aligned} \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + ABC &= A(\overline{B}C + \overline{B}\overline{C} + B\overline{C} + BC) \\ &= A(\overline{B}(C + \overline{C}) + B(\overline{C} + C)) = A(\overline{B} + B) = A \end{aligned}$$

**Couple:**

$$\overline{A}\overline{B}C + \overline{A}B\overline{C} = \overline{B}C(A + A) = \overline{B}C$$